

A 45nm Flash Analog to Digital Converter for Low Voltage High Speed System-on-Chips

Dhruva Ghai, Saraju P. Mohanty and Elias Kougianos
VLSI Design and CAD Laboratory (www.vdcl.cse.unt.edu)
Dept. of Computer Science and Engineering
University of North Texas
dvg0010@unt.edu, smohanty@cse.unt.edu, eliask@unt.edu

Presented by Dhruva Ghai
University of North Texas
dhruva@unt.edu



Outline

- Introduction and Motivation
- Specifications
- Related Research Works
- Design of flash ADC
- The TIQ principle
- TIQ Comparator
- Sizing of transistors
- Functional Simulation
- Ideal vs Actual Characteristics
- DNL
- INL
- SNDR
- Instantaneous Power Plot
- Conclusion and Future Works



Introduction and Motivation

- ❑ ADCs are interfaced with digital circuits in mixed signal chips, where digital signal processing is performed.
- ❑ Supply voltage decreasing rapidly for digital circuits as technology scales.
- ❑ Analog to digital converters required to be operating with these devices at the same voltages.
- ❑ The proposed design meets both criteria: Low supply voltage ($0.7V$) and technology ($45nm$).

Specifications

- Resolution : 6 bits.
- Technology : 45nm.
- Speed : 1Gs/sec.
- V_{LSB} : 500 μ V.
- V_{DD} : 0.7V.
- INL : 0.46LSB.
- DNL : 0.70LSB.
- SNDR : 31.9dB.

Related Research Works

Reference	Resolution (bits)	Technology (nm)	DNL (LSB)	INL (LSB)	SNDR (dB)	VDD (V)	Power (mW)	Samples/s ec.
Choi 2001	6	350	$<\pm 0.3$	$<\pm 0.3$	32	3.3	545	1.3G
Donovan 2002	6	250	-----	-----	33	2.2	150	400M
Geelen 2001	6	350	<0.7	<0.7	5.6 (ENOB)	3.3	300	1.1G
Lee 2002	6	250	1.04	0.81	-----	2.5	59.91	1.11G
Mehr 1999	6	350	<0.32	<0.2	>5 (ENOB)	3.3	225	500M
Sandner 2005	6	130	<0.4	<0.6	32.5	1.5	160	600M
Scholtens 2002	6	180	-----	0.42	5.7(ENOB)	1.95	328	1.6G




Related Research Works....


Reference	Resolution (bits)	Technology (nm)	DNL (LSB)	INL (LSB)	SNDR (dB)	VDD (V)	Power (mW)	Samples/s ec.
Song 2000	6	350	-0.6	0.7	33.5	1	10	50M
Srinivas 2006	6	350	0.3	0.3	33.6	3.3	50	160M
Tseng 2004	6	250	<±0.1	<±0.4	32.7	2.5	35	300M
Uyttenhove 2000	6	350	-----	-----	32	3.3	-----	1G
Uyttenhove 2002	6	250	0.42	0.8	32	1.8	600	1.3G
Yoo 2001	6	250	-----	-----	-----	2.5	66.87	1G
This Work	6	45	0.7	0.46	31.9	0.7	45.42μW	1G



Design of flash ADC

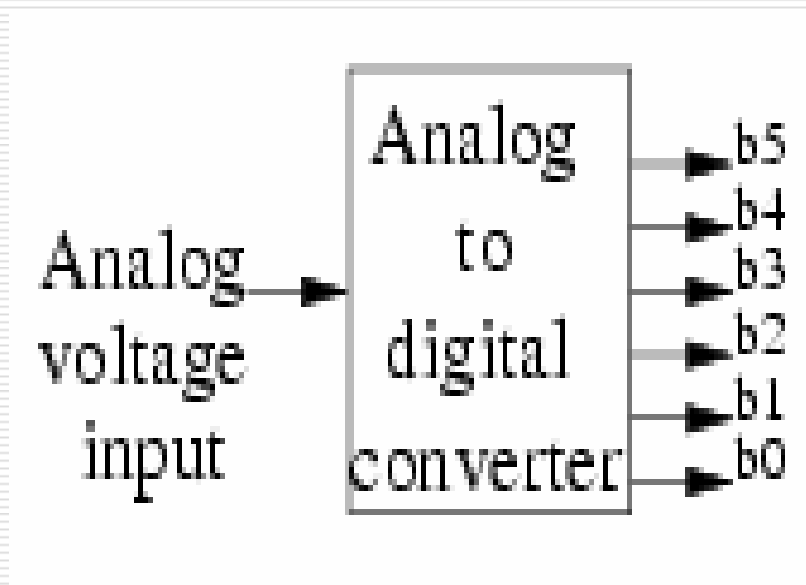

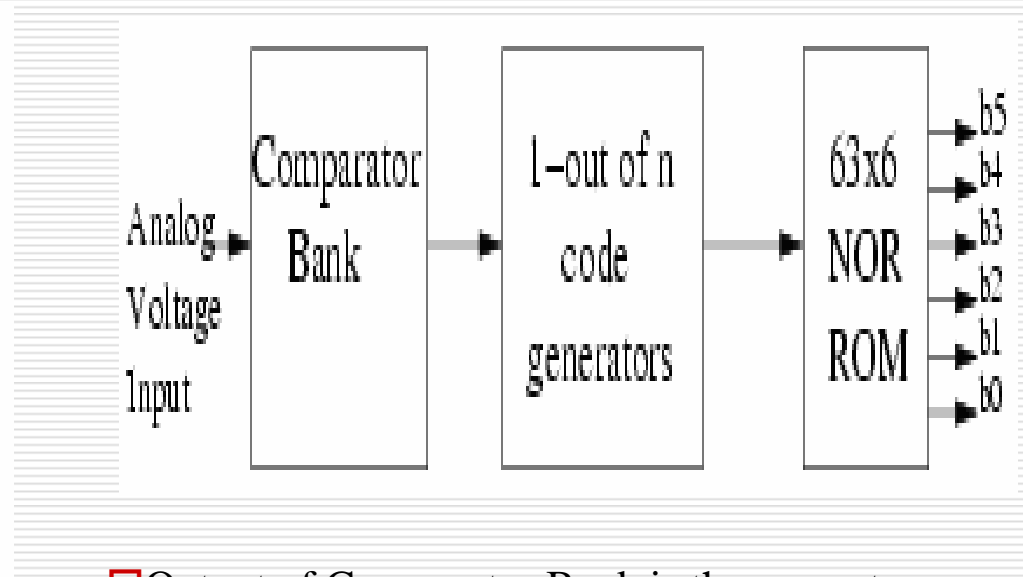
- High level block diagram of ADC.
- Input is analog (generally ramp or sine wave).







- Output of Comparator Bank is thermometer code.
- Converted to 1-out of n code using 1-out of n code generators.
- NOR ROM converts the 1-out of n code to binary code.

Design of flash ADC

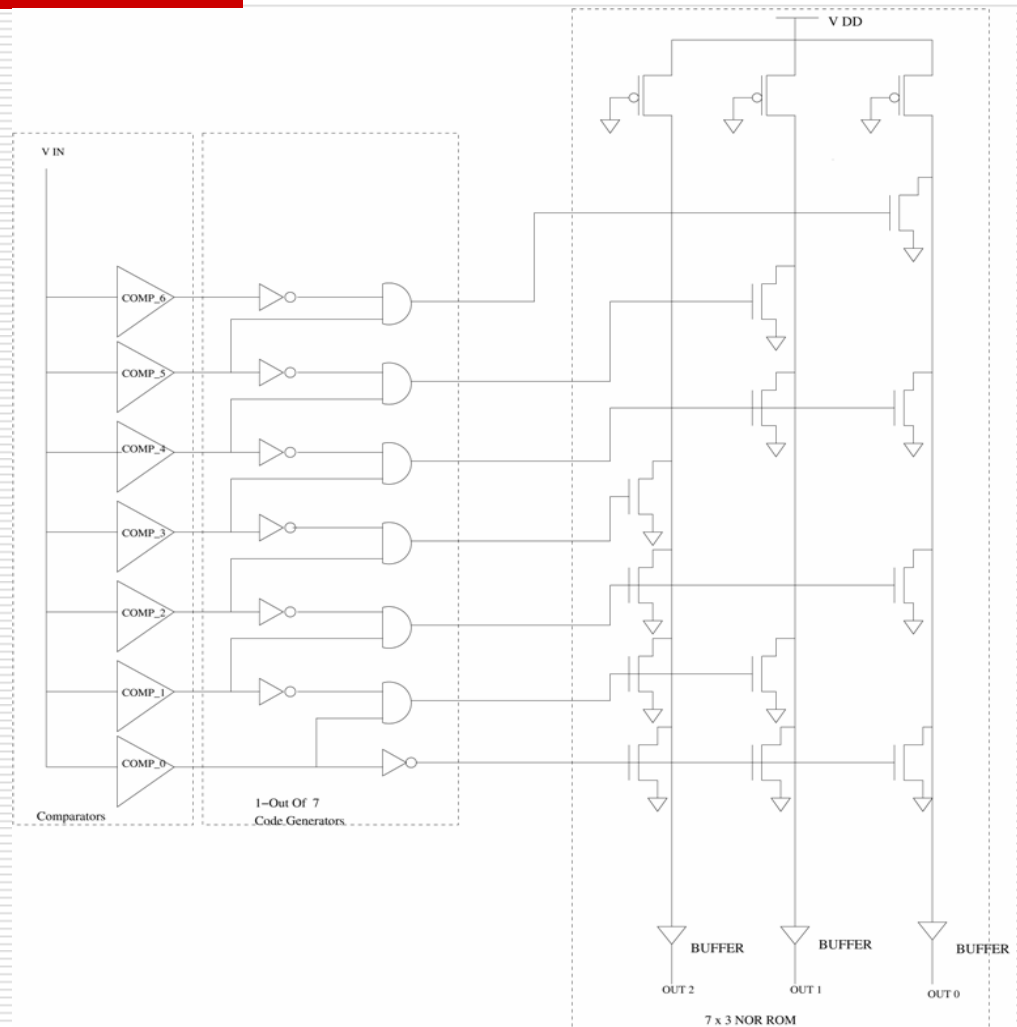- ❑ For an n-bit ADC we need:
 $2^n - 1$ Comparators.
- ❑ 1-out of n code generators.
- ❑ NOR ROM : $2^n - 1 \times n$.
- ❑ For discussion purposes, 3-bit flash ADC is shown. 6-bit ADC has similar structure.



   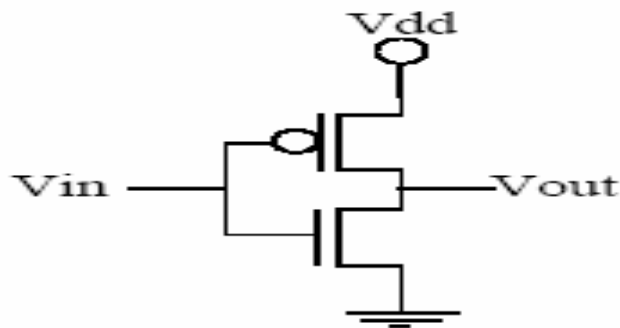
Threshold Inverter Quantization Principle



- ❑ TIQ comparator.
- ❑ Formed by cascading of digital inverters.
- ❑ Sizing of transistors determine switching point.


- ❑ Differential comparator.
- ❑ Require resistive ladder network.
- ❑ Area overhead increases.

TIQ Comparator

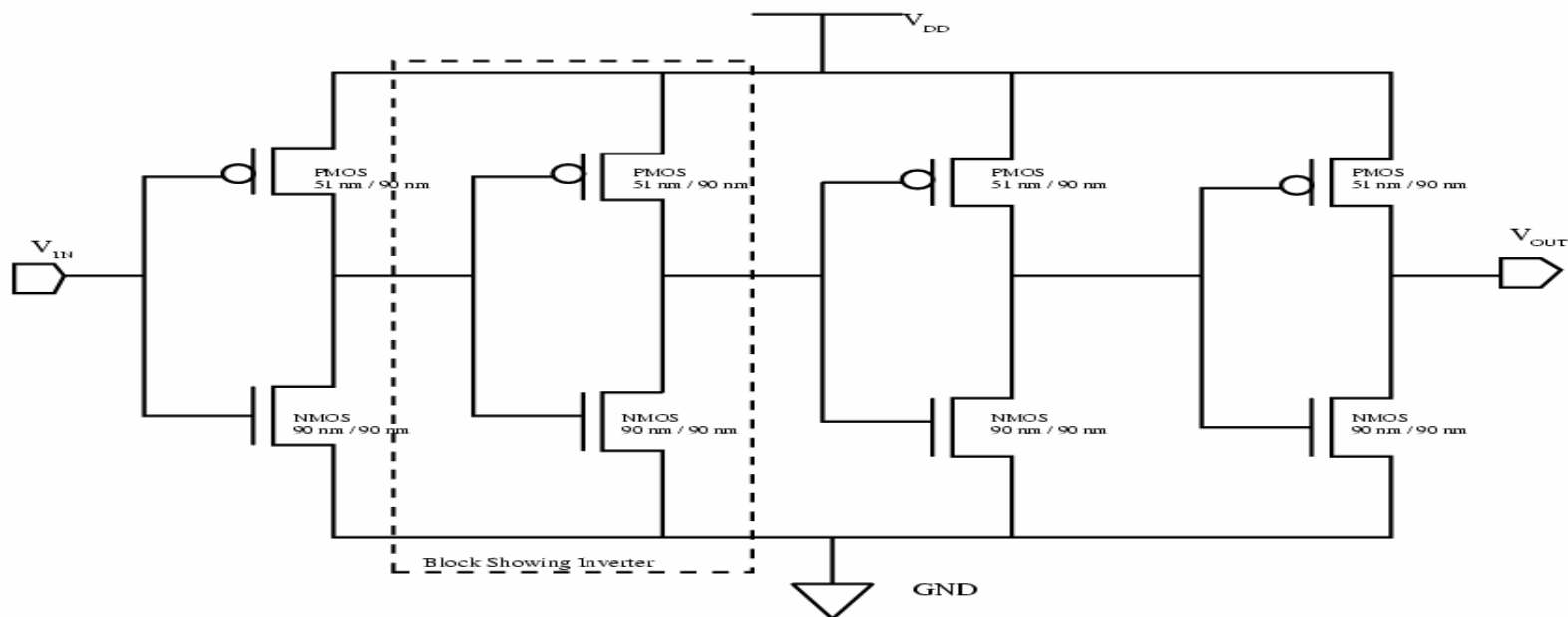


- ❑ Formed by four cascaded inverters.
- ❑ Provide a sharper switching for the comparator and full voltage swing.
- ❑ Sizes of PMOS and NMOS in a comparator are same, but different for different comparators.

Transistor sizing

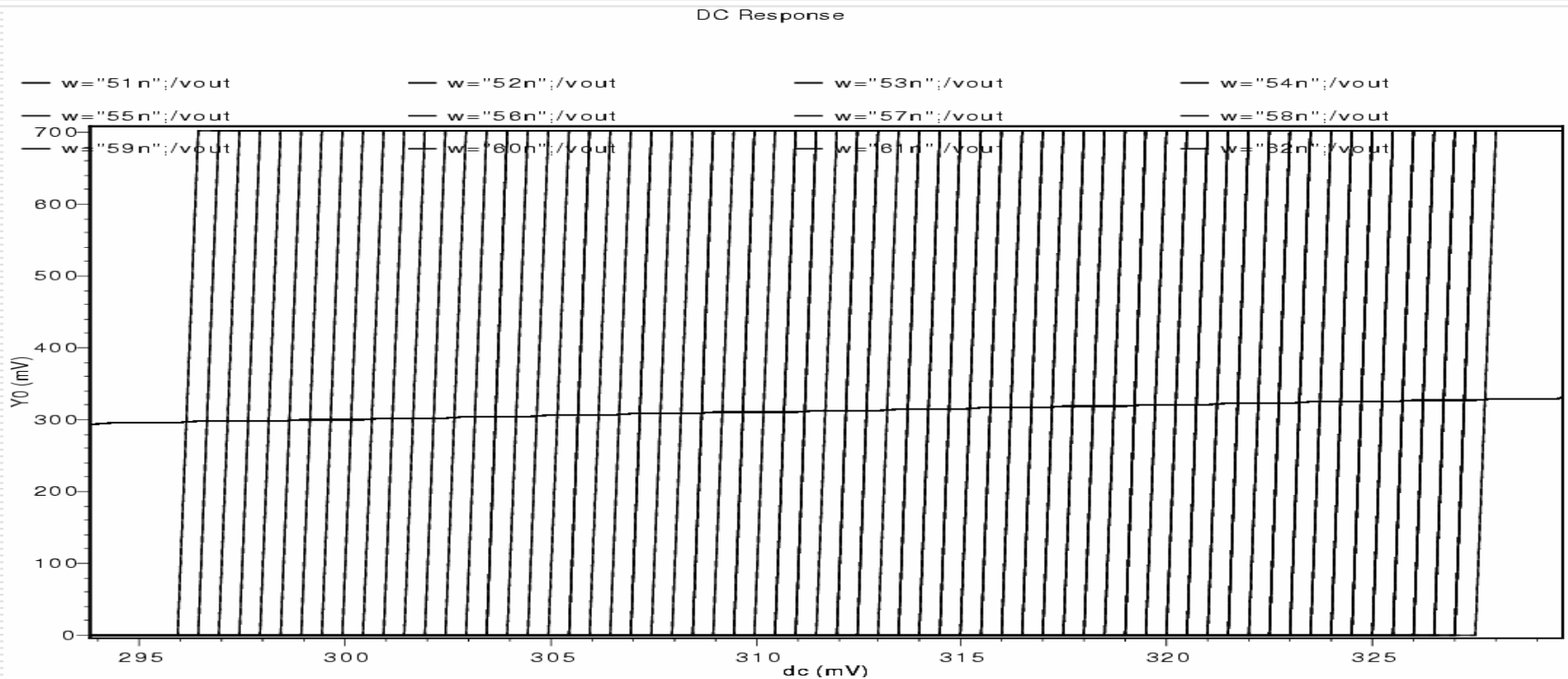


- DC parametric sweep is used to determine the transistor sizes.
- Input voltage varied from 0 to 0.7V in steps of $500\mu V$.
- W/L for NMOS transistors kept as $90nm/90nm$. L for PMOS transistors kept as $90nm$. W for PMOS transistors was given a parametric sweep in steps of $1nm$. Minimum width= $51nm$, maximum width= $163nm$.

Functional Simulation

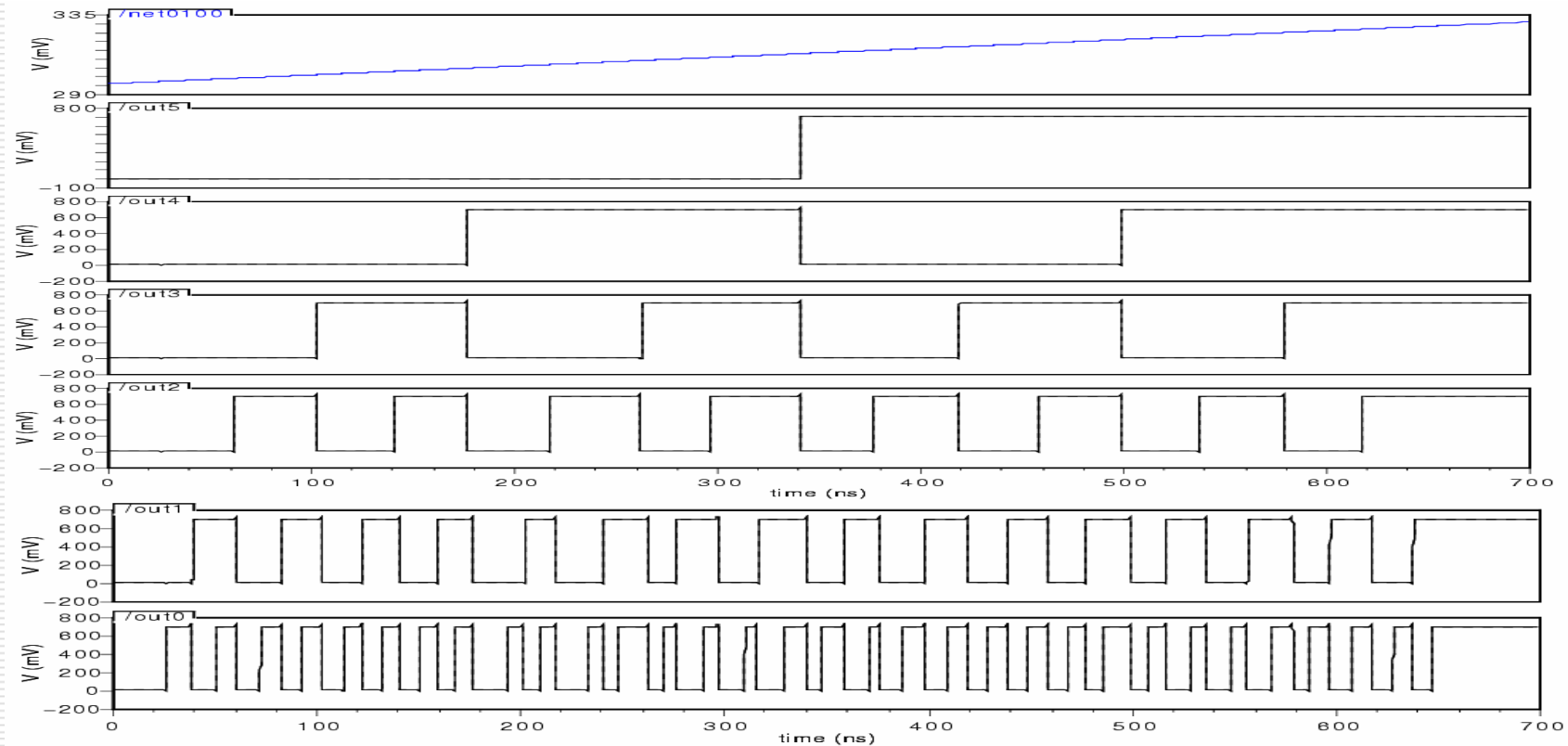


- ❑ Transient analysis carried out.
- ❑ Ramp generated from 296.3mV to 327.8mV . Digital codes going from 0 to 63 are obtained at the output.

Ideal vs Actual Characteristics

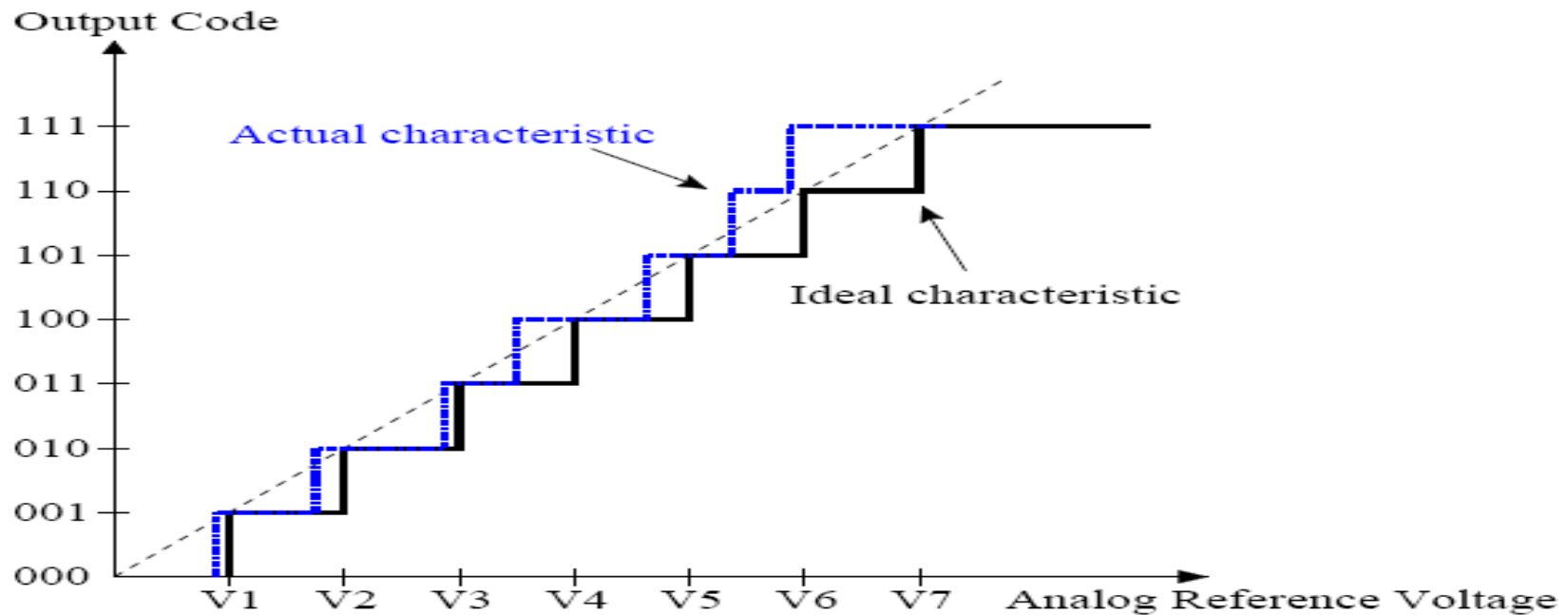

- ❑ Ideal vs actual transfer function
- ❑ Due to transistor implementation, actual transfer function never equal to ideal transfer function.
- ❑ Characterized using DNL and INL.


Max DNL of ADC = $0.7LSB$

 

□ Differential Non-Linearity. Difference between actual step width and ideal value of $1LSB$.


□ Modeled as Verilog-A block. Uses histogram method. $DNL < 1LSB$ ensures monotonicity.

Max INL of ADC = $0.46LSB$

 


- Integral No-linearity. Deviation of actual transfer function from a straight line. expressed in *LSB*.
- Verilog-A block used. Slowly varying ramp given as input, covering full scale range in 4096 steps.

SNDR = 31.9dB

 

- Signal to noise and distortion ratio.
- ADC output fed to Ideal DAC. FFT of DAC output obtained. SNDR calculated from this.

Instantaneous Power Plot

 

- Peak Power= $45.42\mu W$.
- Avg. Power= $8.8\mu W$.
- Low power design.

Conclusion and Future Works

- ❑ Successful ADC design at nano-scale ($45nm$) technology.
- ❑ $DNL=0.7LSB, INL=0.46LSB$.
- ❑ $SNDR=31.9dB$, Low power design (Avg. Power = $8.8\mu W$).
- ❑ Layout using $90nm$ general process design kit.
- ❑ Scaling the layout rules to perform layout at $45nm$.