

# Lecture 8: Process Variation Tolerant Sense Amplifier Design

CSCE 6933/5933

Advanced Topics in VLSI Systems

**Instructor:** Saraju P. Mohanty, Ph. D.

**NOTE:** The figures, text etc included in slides are borrowed from various books, websites, authors pages, and other sources for academic purpose only. The instructor does not claim any originality.




# Outline

- Introduction
- Related Prior Research
- Functional Design of Sense Amplifier Circuits
- Design Optimization – Dual Oxide Technique
- Design Optimization – Dual Threshold Voltage Technique
- Conclusions



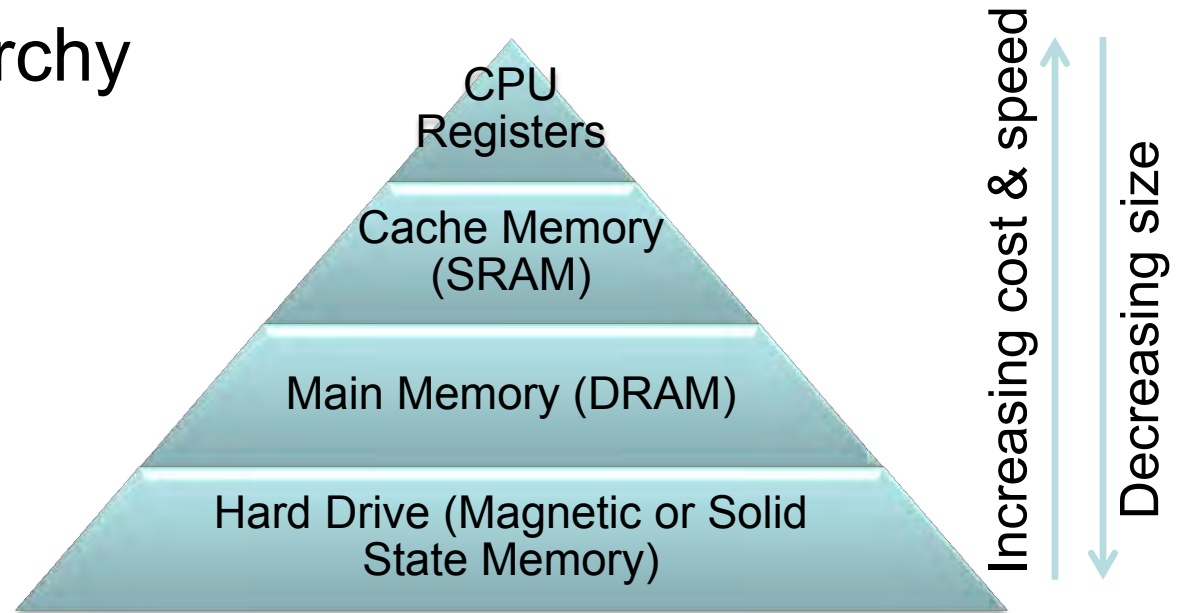
# Introduction

- Dynamic Random Access Memories (DRAMs) are important parts of computing systems
- Relatively fast but not as fast as SRAMs
- Densely Packed
  - 4 times denser than SRAM
- Memory Hierarchy



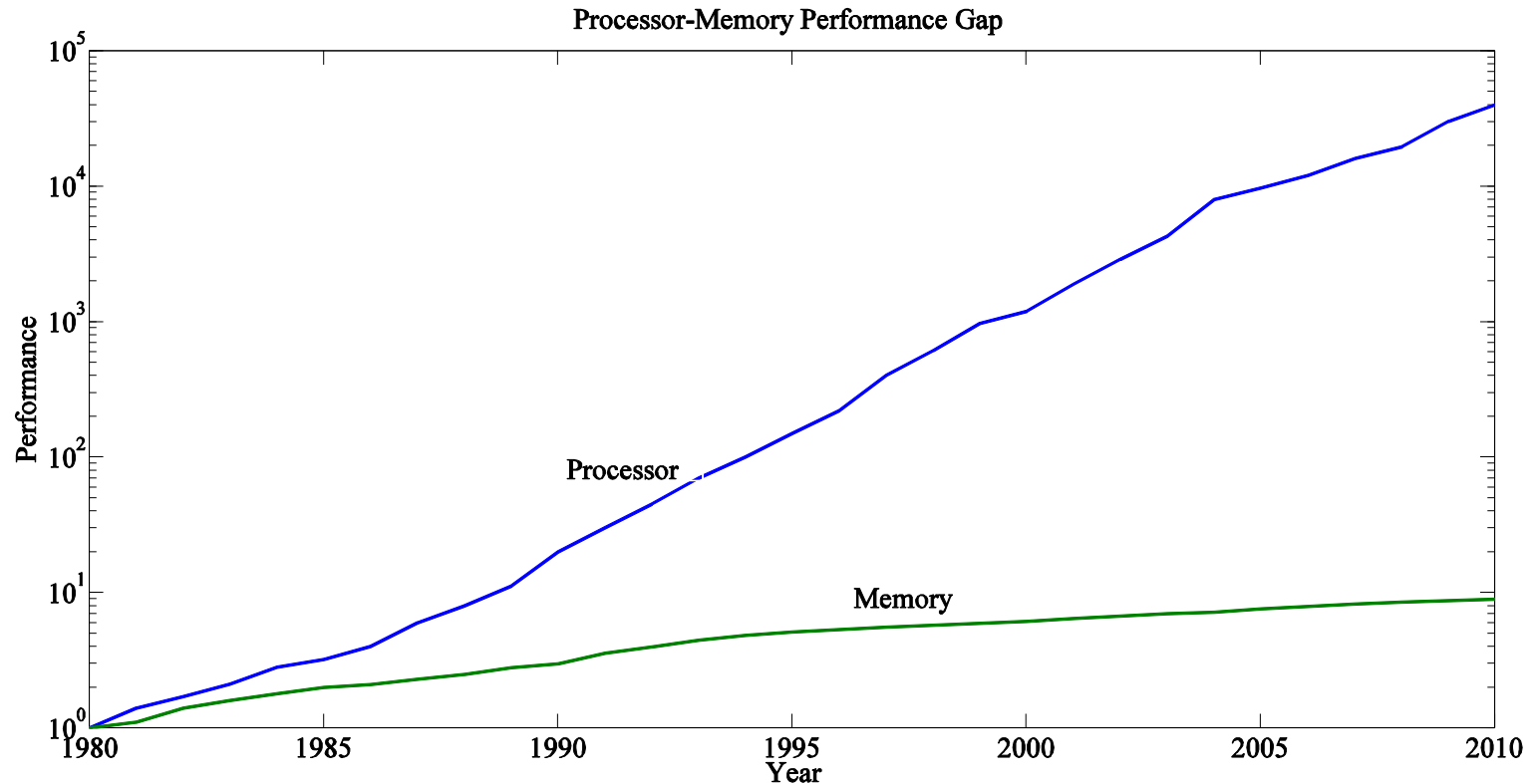
# Motivation

- Memory keeps lagging CPU speed performance



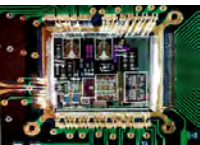
# Introduction: Background

- Historical background
- 1K DRAM designed in 1970
  - Used 3-T cells
- 4Kb – 64Mb DRAM
  - Used 1T-1C cells
  - CMOS technology
  - Multiplexed addressing
- Gb-SDRAM Era (Current Technology)
  - Access synchronized with master clock




# Background

- Basic Organization of DRAM

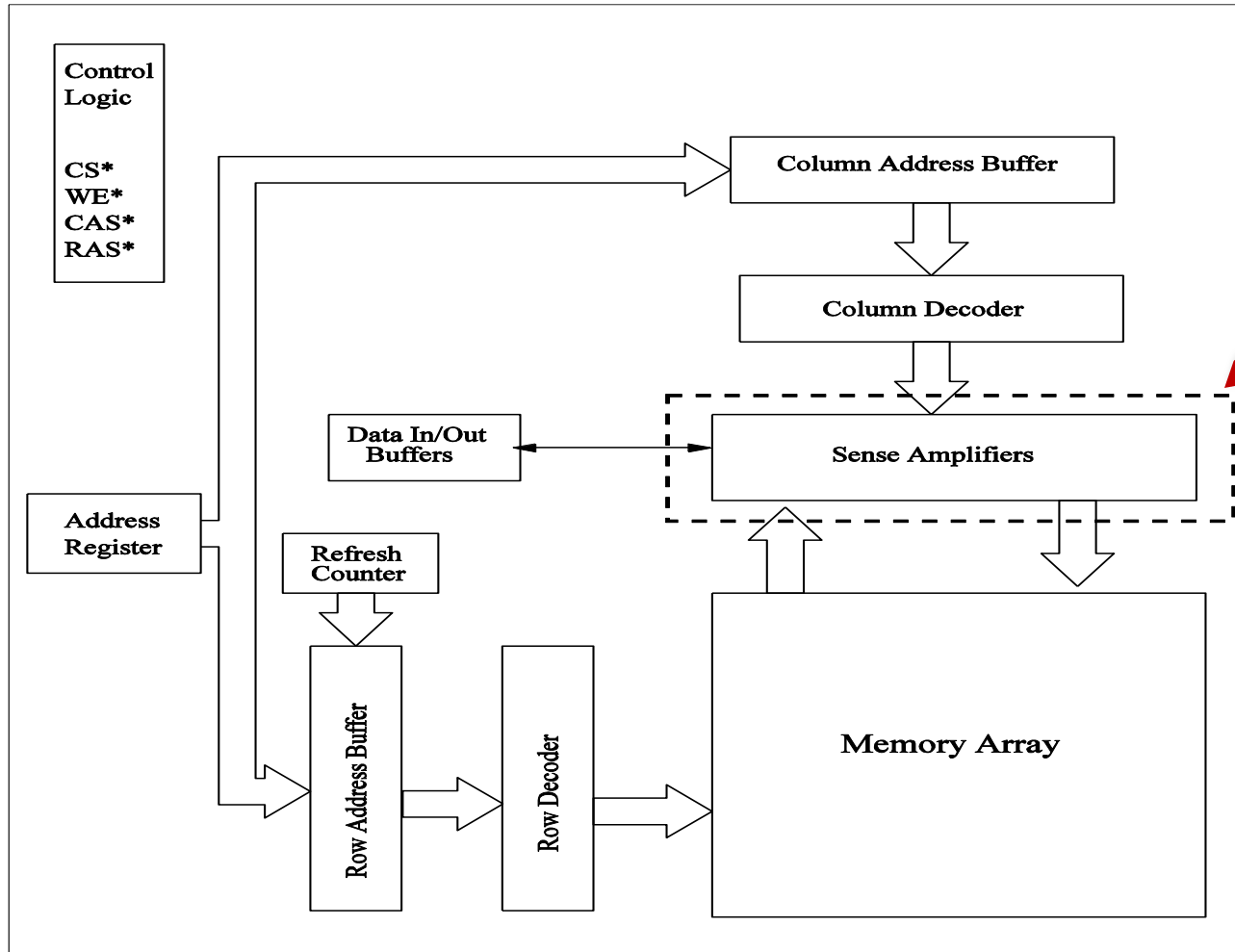


Focus of  
this thesis

 
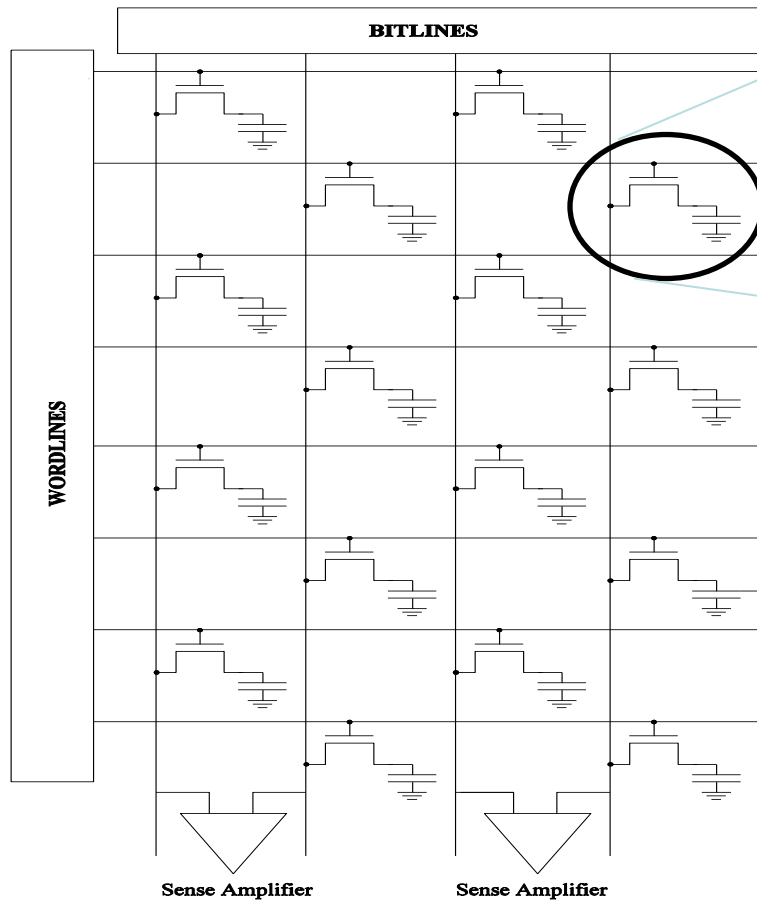
# Memory Array

- ❑ Memory cells of a folded bitline array



- ❑ the word line selects a whole row of cells
- ❑ the bit line reads and writes the capacitor
- ❑ The sense amplifier connects two columns, one serves as a reference cell
- ❑ All columns are active on a row access



# Sense Amplifier: Background and Operation


- Major Functionality:
  - Detect and amplify voltage change
  - Refresh circuit
  - Act as column buffers
- Basic Access Operations
  - To access (read or write to a cell) there are three basic operations performed – the precharge, row and column access.
  - The precharge phase charges all bitlines to a determined voltage, usually  $V_{DD}/2$ .




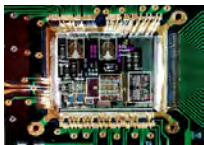
# Sense Amplifier: Background and Operation

- For a read operation,
  - The row access activates the wordline of the cell and all the capacitors begin to share charge with the bitlines.
  - Sense amplifiers sense and magnify voltage changes.
  - The data from the sense amplifier is selected by the column bit during the column access.
- Write Operation.
  - The row access activates the wordlines.
  - The bitline drives the the cell to a “0” or “1” depending on the value to be written.
- Refresh Operation: This is done by reading every address of the DRAM.




# Issues in Nanoscale DRAM Circuit Design

- Variability: Variability in process and design parameters becomes more acute due to scaling technologies and processes
- Leakage: Leakage is increasing due to scaling of oxide thickness
- Power Consumption : current leakage increases the static power consumption


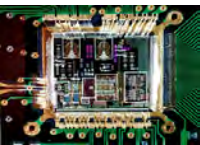
# Process Variation

- Process variations occur due to different manufacturing environments and process difficulty
- The effects of the process variation result in varying device parameters including:
  - supply voltage,
  - threshold voltages,
  - oxide thickness,
  - transconductance,
  - channel lengths,
  - channel widths, and
  - source and drain doping concentration



# Process Variations Classifications

## Global Variations

Fabrication  
Process

Lot  
Process

Wafer  
Process

From plant  
to plant


From lot to  
lot in a plant

From wafer  
to wafer in a  
lot


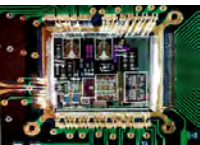
# Salient Points of this Design Flow

- Analysis of effects of device parameters on FoMs of a sense amplifier.
- Analysis of effect of process variation on the performance of full latch sense amplifier.
- Design process to limit the effects of process variations with optimizations to FoMs.
- Exploring dual-Tox and dual-V<sub>th</sub> for sense amplifier optimization.



# Related Prior Research

Research	Parameter	Feature	Approach	Result Improvement
Sherwin	$V_{DD}$	Voltage gain	Physical measurements	-
Chow	$C_{BL}$	Sense Speed	Spice simulations	Sense speed – 40%
Laurent	$C_{BL}, V_{th}, \beta$	Signal Margin	Spice Simulations	-
Vollrath	$C_{BL}, V_{th}, \beta$	Signal Margin	Physical measurements	-
Choudhary	$V_{th}, L, W$	Yield	Monte Carlo analysis	Improved Yield
Hong	-	Sense scheme	Spice simulations	Improved sense amplifier cell ration
Singh		SE rise time	Spice simulations	Eliminated offset voltage
This research	Dual- $V_{th}$	Process variability	Optimization	Sense delay – 80.2% Sense margin – 61.9%



# Sense Amplifiers Topologies

- Voltage Based Sense Amplifiers
  - Sense and amplify a small differential voltage
  - Variations include cross couple and full latch cross couple
- Current Based Sense Amplifiers
  - Sense and amplify small differential currents
  - Lower input capacitance
  - Includes current-mirror, clamped bitline current amplifier



# Functional Design of Sense Amplifier


- Two cross coupled inverters
- The major parts of the full latch voltage sense amplifier are
  - Nsense Amps
  - Psense Amps
  - Precharge and Equalization Circuits






# Nsense and Psense Amplifiers

## □ Nsense amplification

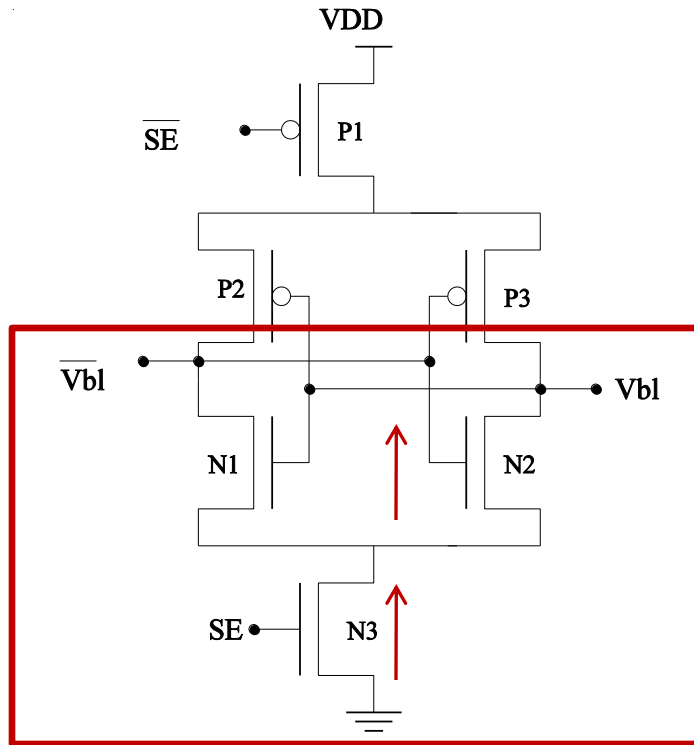


- Nsense amplifiers activated by SE through N3
- N2 begins to conduct and eventually pulls  $V_{bl}$  to ground


## □ Psense amplification

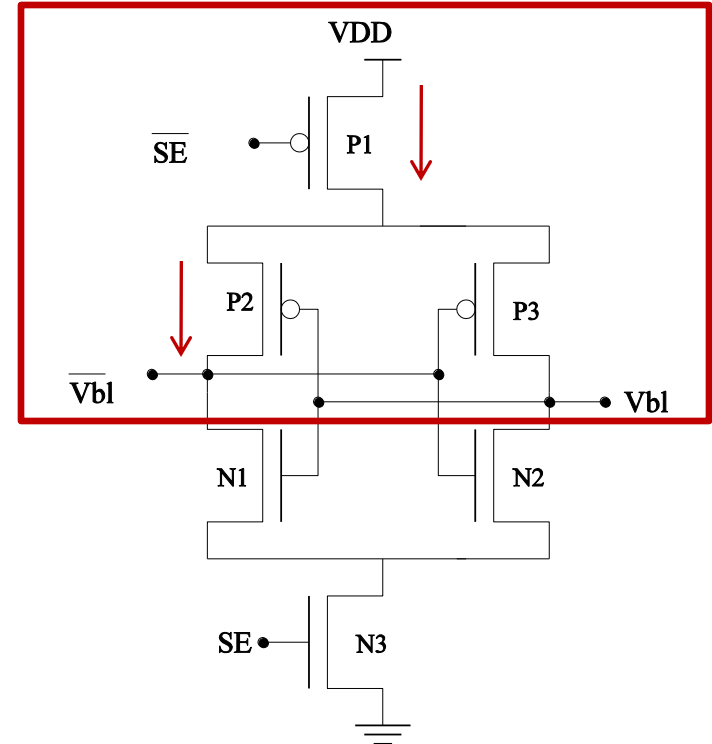

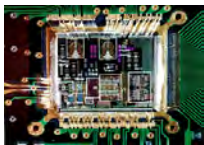- Psense amplifiers activated by SEbar through P1
- P2 begins to conduct and eventually pulls  $V_{bl}$  bar to ground




# Precharge Circuit

 

- ❑ When PRE signal goes high, Vbl and Vblbar are charged to VDD/2 through M1 and M2  
P sense amplifiers activated by P1
- ❑ M3 Helps to speed up the process



# Functional Design of Sense Amplifier

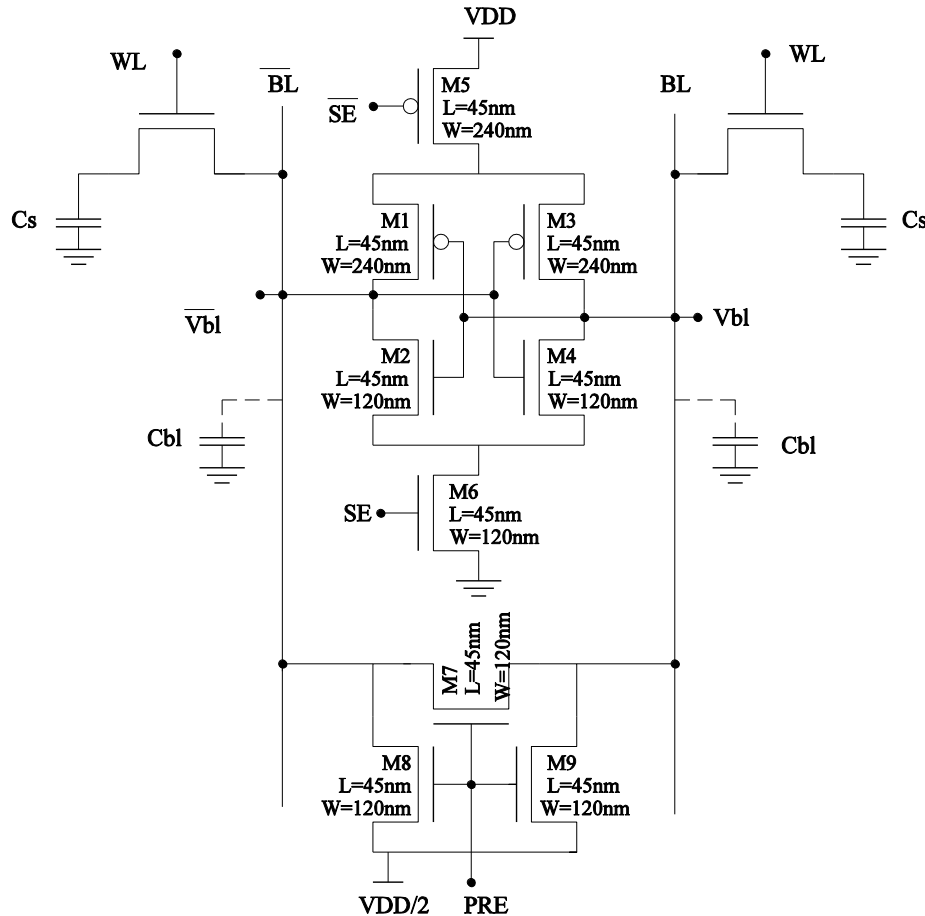

Equations for Charge Sharing


$$\Delta V = \frac{C_S}{C_S + C_{BL}} \left( V_{CS} - \frac{V_{DD}}{2} \right)$$

when bit cell value is 1,  $V_{CS} = V_{DD} - V_{th}$


$$\Delta V \approx \frac{C_S}{C_{BL}} \left( \frac{V_{DD}}{2} - V_t \right)$$

when bit cell value is 0,  $V_{CS} = 0$

 
$$\Delta V \approx -\frac{C_S}{C_{BL}} \left( \frac{V_{DD}}{2} \right)$$


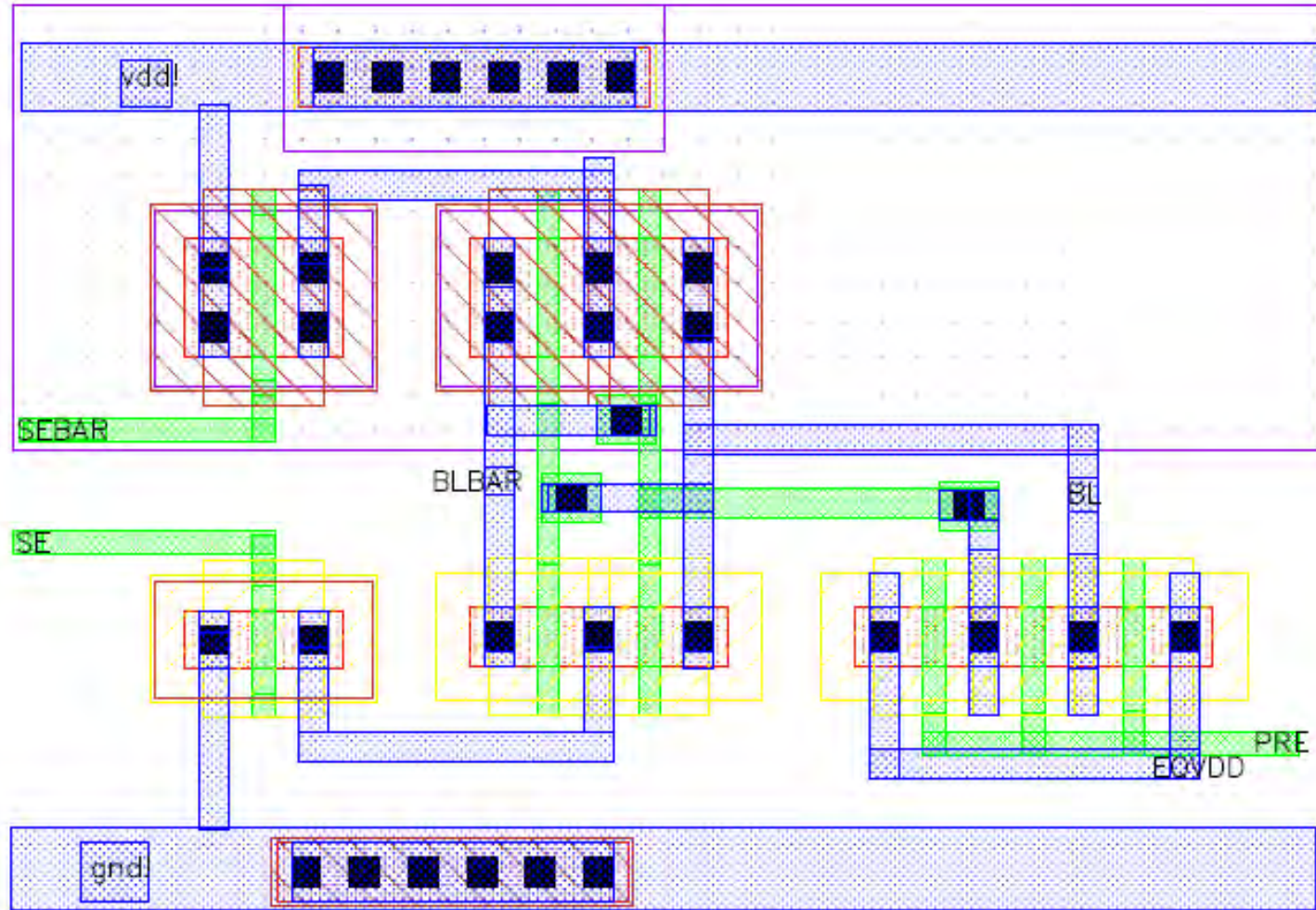
# Physical Layout for 45nm Sense Amplifier



# Waveform Simulation

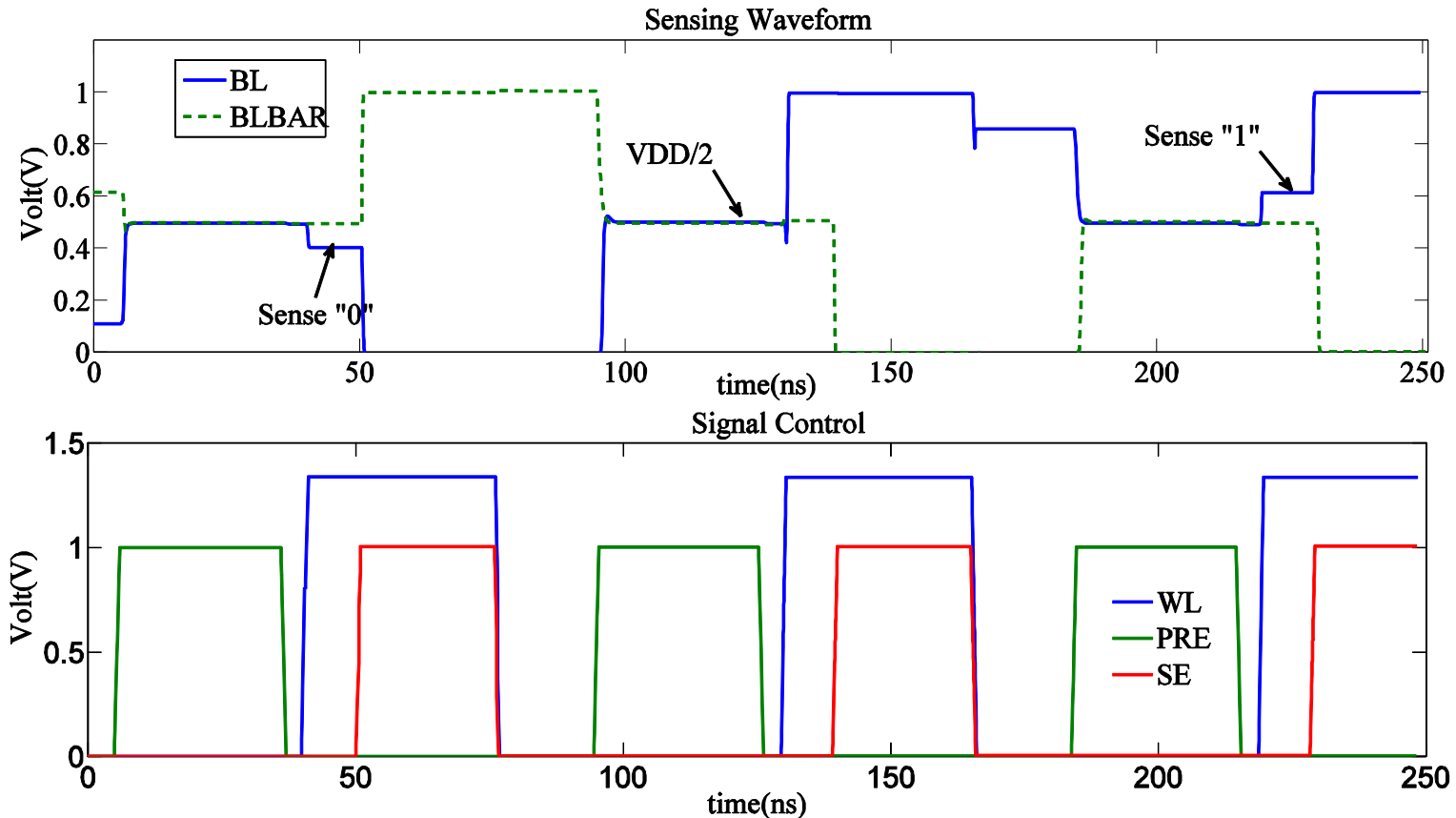


# Figures of Merit

- Precharge and Equalization Time
- Average Power Consumption
- Sense Delay
- Sense Margin

Table for Figures of Merit Characterization


FoM	Precharge	Power	Sense Delay	Sense Margin
Value	7.50 ns	153.101 mW	4.39 ns	43.46 mV

 




 
# Parametric Analysis

The following parameters analysed

- Gate Lengths and Widths ( $L_n$ ,  $L_p$ ,  $W_n$ ,  $W_p$ )
- Voltage Supply ( $V_{DD}$ )
- Cell Capacitance ( $C_S$ )
- Bitline Capacitance ( $C_{BL}$ )
- Oxide Thickness ( $T_{oxn}$ ,  $T_{oxp}$ )
- Threshold Voltage ( $V_{thn}$ ,  $V_{thp}$ )







# Sensitivity of FoMs on Ln

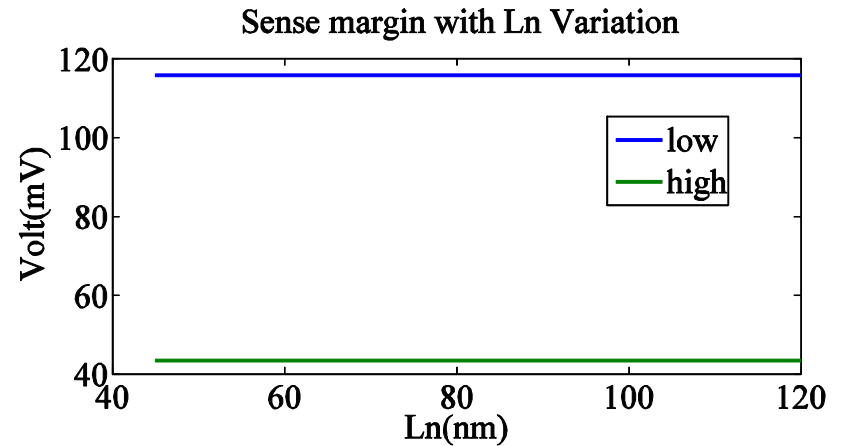
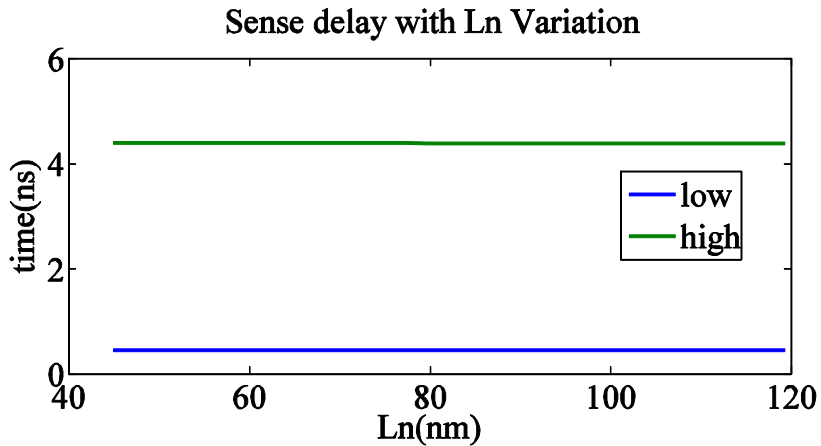
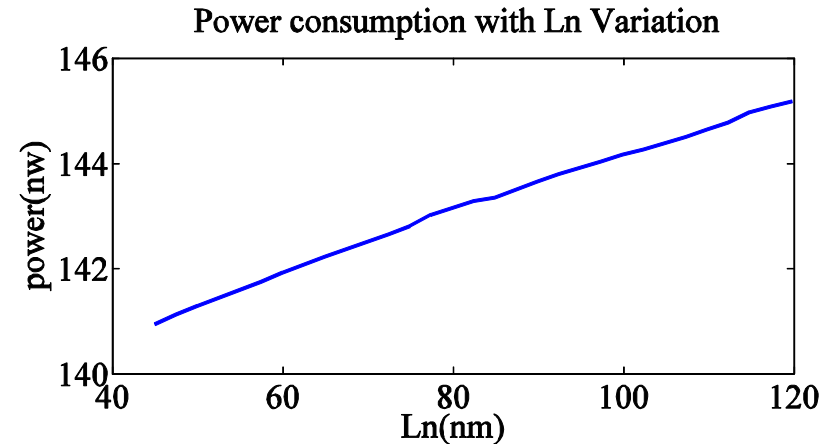
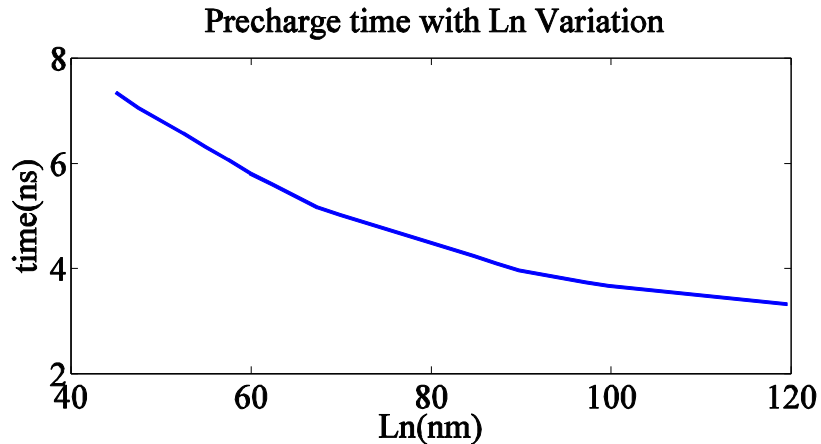




# Sensitivity of FoMs on Lp

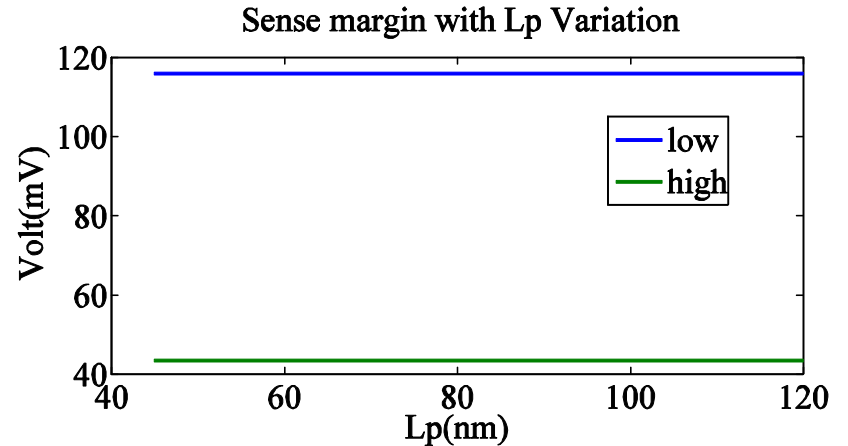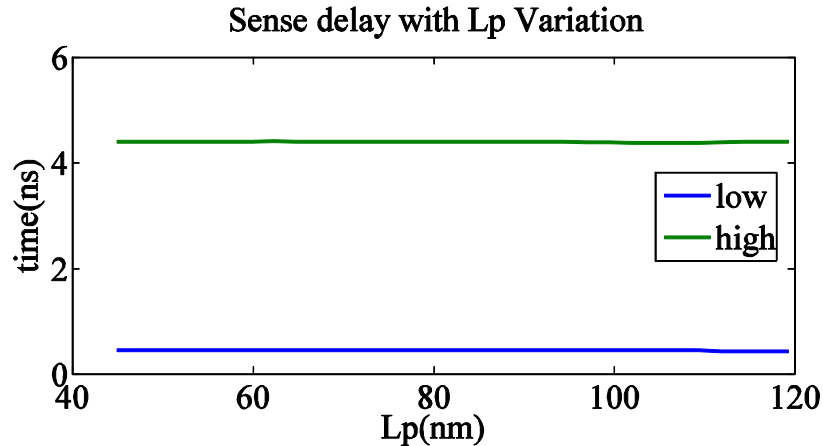  


# Sensitivity of FoMs on Wn

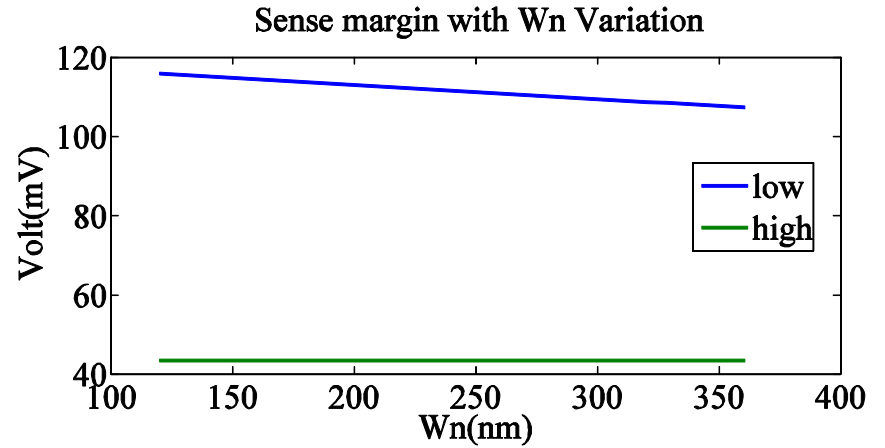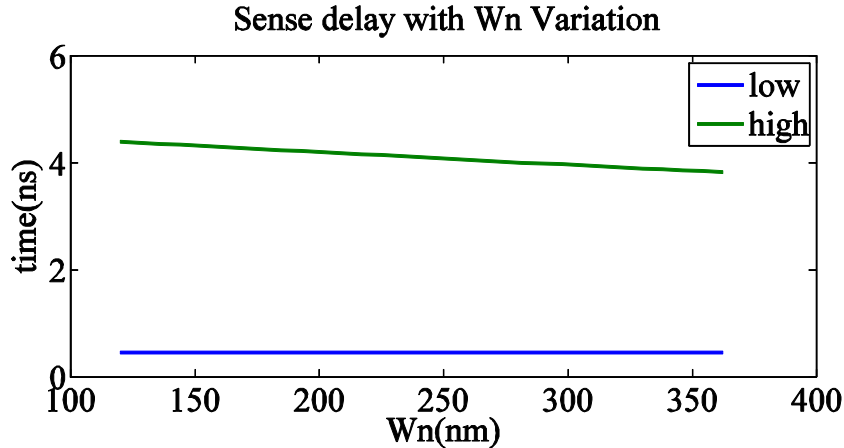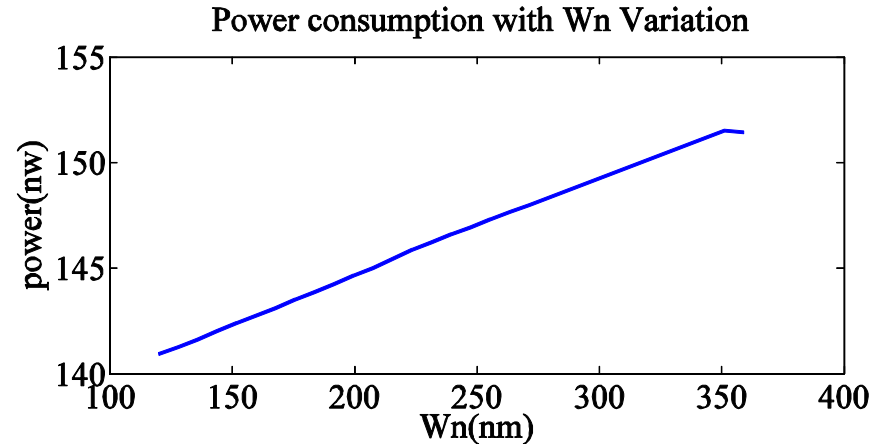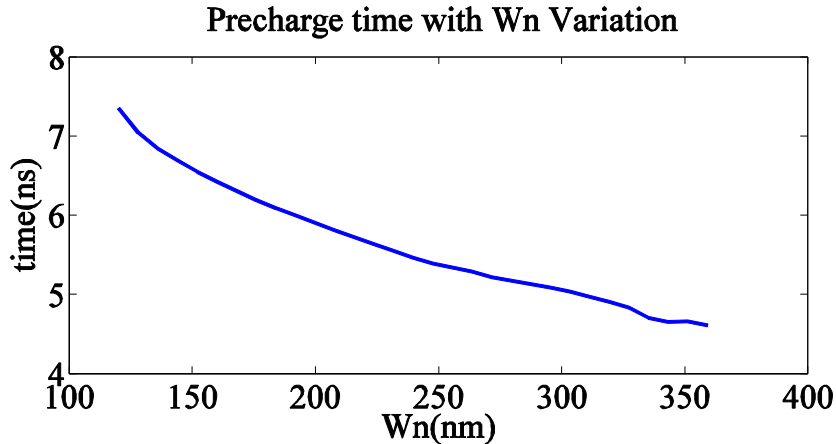


# Sensitivity of FoMs on Wp


Precharge time with Wp Variation

 


Power consumption with Wp Variation

 

Sense delay with Wp Variation

 


Sense margin with Wp Variation

 

# Summary of Effects of Parameter Variations on FoMs


- Table of Parameter Variations

Parameter	Precharge	Power	Sense Delay	Sense Margin
$L_n$	decrease	increase	mild decrease	mild increase
$L_p$	increase	decrease	mild decrease	mild decrease
$W_n$	decrease	increase	decrease	decrease
$W_p$	increase	increase	mild decrease	decrease
$V_{DD}$	decrease	increase	decrease	increase
$C_S$	increase	increase	decrease	increase
$C_{BL}$	increase	increase	mild increase	decrease
$V_{thn}$	increase	decrease	increase	mild decrease
$V_{thp}$	increase	decrease	increase	mild decrease
$t_{oxn}$	decrease	increase	decrease	increase
$t_{oxp}$	decrease	decrease	mild decrease	mild increase




 

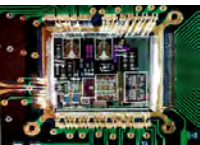
# Dual Oxide Technology

- A Monte Carlo analysis of the effects of process variation of design parameters on FoMs
  - Parameters were varied at +/- 10% of selected values from parametric analysis
- A Monte Carlo analysis of the FoMs reaction to variation of individual parameters
- Transistors are assigned different oxide thickness for optimizing design
  - $T_{\text{ox,high}} = 3\text{nm}$
  - $T_{\text{ox,low}} = 2.4\text{nm}$
- FoM's are analyzed with different oxide thickness




# Monte Carlo Analysis: PDF of FoMs

    


# Probability Density Function of Different FoMs of the Sense Amplifier

Params	Precharge PDF		Power PDF		Sense Delay PDF		Sense Margin PDF	
	$\mu$ (ps)	$\sigma$ (ps)	$\mu$ (nW)	$\sigma$ (nW)	$\mu$ ( $\mu$ s)	$\sigma$ (ps)	$\mu$ (mV)	$\sigma$ ( $\mu$ V)
$L_n$	773.65	13.81	191.67	0.56	1.26	16.79	10.67	32.22
$L_p$	773.44	2.40	191.67	0.06	1.26	0.15	10.68	2.22
$W_n$	773.18	5.04	191.71	0.50	1.25	15.82	10.67	102.41
$W_p$	774.08	6.34	190.69	2.07	1.26	0.22	10.68	13.49
$V_{DD}$	772.72	123.68	190.85	27.25	1.30	0.36	10.21	2074.63
$C_S$	772.61	0.20	191.68	0.25	1.26	49.81	10.66	367.51
$C_{BL}$	773.48	14.76	191.73	6.38	1.26	3.76	10.69	591.49
$t_{oxn}$	774.15	11.68	191.32	1.47	1.26	25.48	10.62	311.87
$t_{oxp}$	773.74	2.05	192.06	1.93	1.26	0.10	10.68	65.80

 

# Flow Diagram

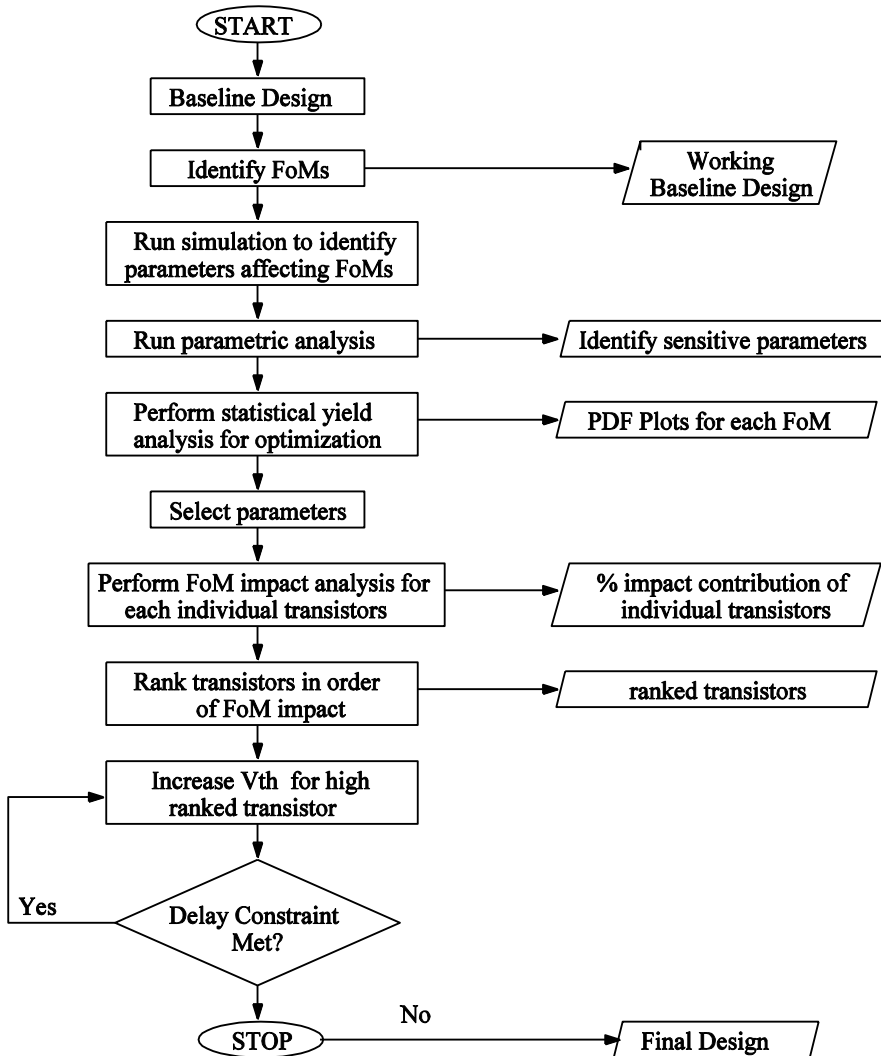



---

**Algorithm 1** Heuristic algorithm for sense amplifier optimization using Dual Oxide Based Technology

---

 - 1: Create the netlist of the sense amplifier circuit.
  - 2: Number each of the transistors in the netlist from 1 to N.
  - 3: **for** Each of the transistors  $i = 1$  to N **do**
  - 4: Rank the transistors for a figure of merit. For example, contributions to precharge.
  - 5: Identify the significant transistors from the ranks, e.g. 30% or 50%
  - 6: **end for**
  - 7: Start with the highest ranked transistor as  $i = 0$
  - 8: **while** Design constraint of the sense amplifier is met and the transistor  $M_i$  is a significant transistor that contributes to the overall FoM value of the sense amplifier **do**
  - 9: Increase thickness oxide of the the transistor  $M_i$
  - 10: Move to the next ranked transistor
  - 11: **end while**
- 










# Dual Threshold Voltage Technology

- A Monte Carlo analysis of the effects of process variation of design parameters on FoMs
  - Parameters were varied at +/- 10% of selected values from parametric analysis
- A Monte Carlo analysis of the FoMs reaction to variation of individual parameters
- Transistors are assigned different threshold voltages for optimizing design
  - $V_{th,high} = 0.36V$
  - $V_{th,low} = 0.18V$
- FoM's are analyzed with different threshold voltages



# PDF of FoMs

    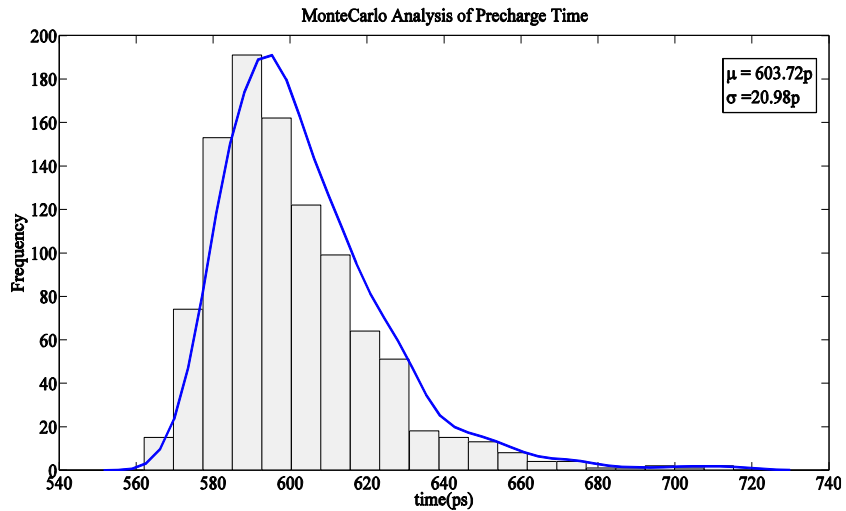


# Probability Density Function of Different FoMs of the Sense Amplifier

Params	Precharge PDF		Power PDF		Sense Delay PDF		Sense Margin PDF	
	$\mu$ (ps)	$\sigma$ (ps)	$\mu$ (nW)	$\sigma$ (nW)	$\mu$ ( $\mu$ s)	$\sigma$ (ps)	$\mu$ (mV)	$\sigma$ ( $\mu$ V)
$L_n$	598.01	4.22	94.93	3.13	770.10	80.85	7.89	907.49
$L_p$	597.92	4.12	94.20	3.08	770.12	80.85	7.88	914.88
$W_n$	598.20	5.47	94.16	3.03	770.20	81.01	7.87	920.6
$W_p$	597.93	4.16	94.15	3.25	770.12	80.86	7.88	913.22
$V_{DD}$	602.37	17.83	94.59	16.88	803.06	211.95	6.93	3154.05
$C_S$	597.93	4.15	94.18	3.02	769.13	89.73	7.87	943.99
$C_{BL}$	597.82	6.16	94.11	4.11	770.41	81.40	7.91	999.44
$V_{thn}$	598.69	5.93	94.42	3.12	774.26	98.08	7.89	1007.7
$t_{oxn}$	598.19	5.09	94.36	3.53	773.61	90.90	7.82	1220.27
$t_{oxp}$	598.11	4.20	94.41	3.09	771.42	85.22	7.96	1003.42



# Flow Diagram/Algorithm

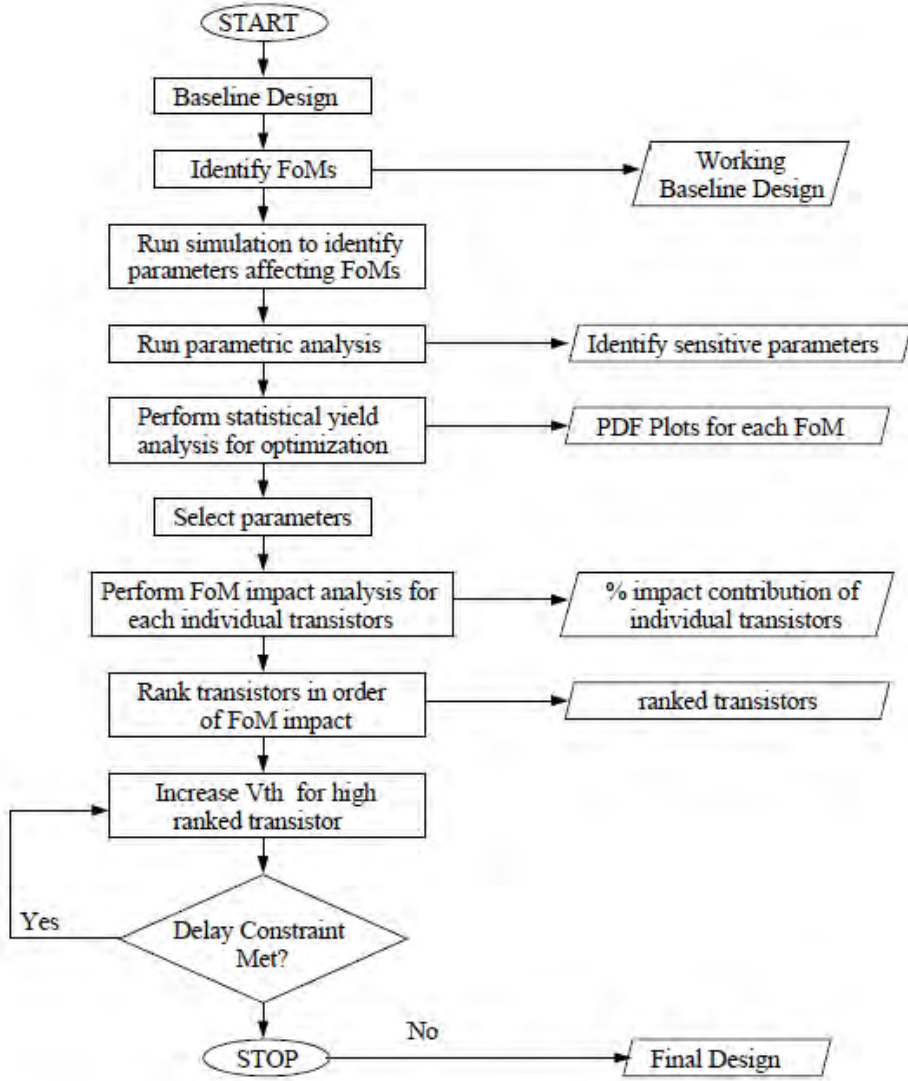

---

**Algorithm 2** Heuristic algorithm for sense amplifier circuit optimization using Dual Threshold Based Technology

---

- 1: Create the netlist of the sense amplifier circuit.
  - 2: Number each of the transistors in the netlist from 1 to N.
  - 3: **for** Each of the transistors  $i = 1$  to N **do**
  - 4: Rank the transistors for a figure of merit. For example, contributions to precharge.
  - 5: Identify the significant transistors from the ranks, e.g. 30% or 50%, etc
  - 6: **end for**
  - 7: Start with the highest ranked transistor as  $i = 0$
  - 8: **while** Design constraint of the sense amplifier is met and the transistor  $M_i$  is a significant transistor that contributes to the overall FoM value of the sense amplifier **do**
  - 9: Increase threshold voltage of the transistor  $M_i$ .
  - 10: Move to the next ranked transistor.
  - 11: **end while**
- 



# Characterization of Optimized Design

- The FoM's are improved on the final design.

FoMs	Precharge	Power	Sense Delay	Sense Margin
Baseline	7.5 ns	153.1 $\mu$ W	4.4 ns	43.4 mV
Dual- $V_{th}$ -Optimal	1.2 ns	133.1 $\mu$ W	0.87 ns	70.4 mV
Improvement	83.9%	13.1%	80.2%	61.9%



# Conclusions

- The effects of process variation were analyzed through parametric and Monte Carlo analysis.
- A method of producing more tolerant and optimal designs was presented.
- FoM's were improved
  - Precharge by 83.9%
  - Sense delay by 80.2%
  - Sense margin by 61.9%
  - Power dissipation by 13.1%
- Analysis will be extended to different sense amplifier topologies.

