


Lecture 11: Efficient Design of Flash ADC

CSCE 6933/5933


Advanced Topics in VLSI Systems

Instructor: Saraju P. Mohanty, Ph. D.

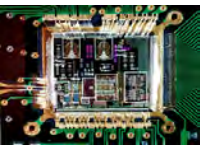NOTE: The figures, text etc included in slides are borrowed from various books, websites, authors pages, and other sources for academic purpose only. The instructor does not claim any originality.




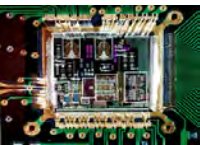A *45nm* Flash Analog to Digital Converter (ADC)




Outline

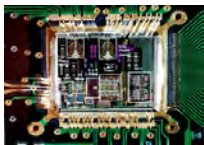- Introduction and Motivation
- Specifications
- Related Research Works
- Design of flash ADC
- The TIQ principle
- TIQ Comparator
- Sizing of transistors
- Functional Simulation
- Ideal vs Actual Characteristics
- DNL
- INL
- SNDR
- Instantaneous Power Plot
- Conclusion and Future Works



Introduction and Motivation

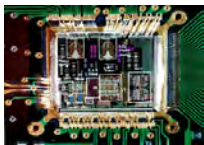- ADCs are interfaced with digital circuits in mixed signal chips, where digital signal processing is performed.
- Supply voltage decreasing rapidly for digital circuits as technology scales.
- Analog to digital converters required to be operating with these devices at the same voltages.
- The proposed design meets both criteria: Low supply voltage ($0.7V$) and technology ($45nm$).




Specifications

- Resolution : 6 bits.
- Technology : $45nm$.
- Speed : $1Gs/sec$.
- V_{LSB} : $500\mu V$.
- V_{DD} : $0.7V$.
- INL : $0.46LSB$.
- DNL : $0.70LSB$.
- SNDR : $31.9dB$.




Related Research Works

Reference	Resolution (bits)	Technology (nm)	DNL (LSB)	INL (LSB)	SNDR (dB)	VDD (V)	Power (mW)	Samples/s ec.
Choi 2001	6	350	$<\pm 0.3$	$<\pm 0.3$	32	3.3	545	1.3G
Donovan 2002	6	250	-----	-----	33	2.2	150	400M
Geelen 2001	6	350	<0.7	<0.7	5.6 (ENOB)	3.3	300	1.1G
Lee 2002	6	250	1.04	0.81	-----	2.5	59.91	1.11G
Mehr 1999	6	350	<0.32	<0.2	>5 (ENOB)	3.3	225	500M
Sandner 2005	6	130	<0.4	<0.6	32.5	1.5	160	600M
Scholtens 2002	6	180	-----	0.42	5.7(ENOB)	1.95	328	1.6G

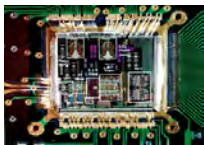


Related Research Works....


Reference	Resolution (bits)	Technology (nm)	DNL (LSB)	INL (LSB)	SNDR (dB)	VDD (V)	Power (mW)	Samples/sec.
Song 2000	6	350	-0.6	0.7	33.5	1	10	50M
Srinivas 2006	6	350	0.3	0.3	33.6	3.3	50	160M
Tseng 2004	6	250	$<\pm 0.1$	$<\pm 0.4$	32.7	2.5	35	300M
Uyttenhove 2000	6	350	-----	-----	32	3.3	-----	1G
Uyttenhove 2002	6	250	0.42	0.8	32	1.8	600	1.3G
Yoo 2001	6	250	-----	-----	-----	2.5	66.87	1G
This Design	6	45	0.7	0.46	31.9	0.7	45.42μW	1G

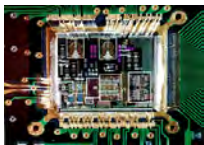

Design of flash ADC

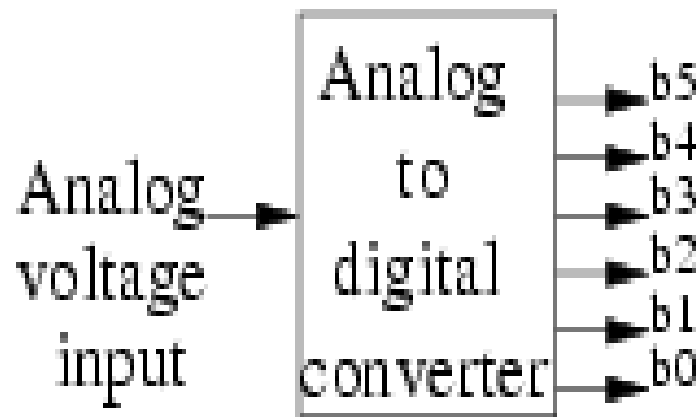

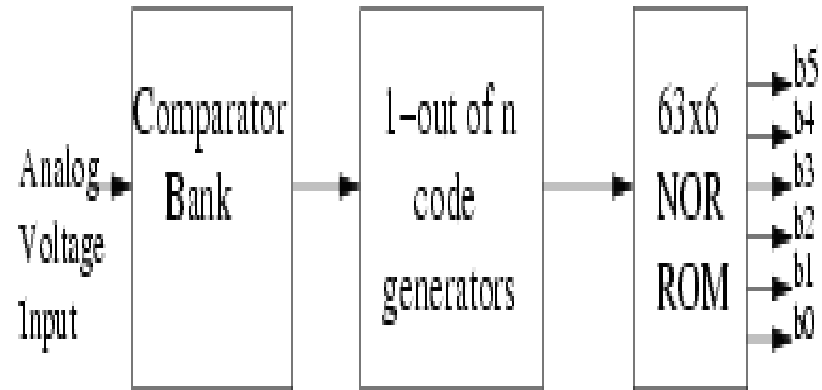- High level block diagram of ADC.
- Input is analog (generally ramp or sine wave).





- Output of Comparator Bank is thermometer code.
- Converted to 1-out of n code using 1-out of n code generators.
- NOR ROM converts the 1-out of n code to binary code.





Design of flash ADC

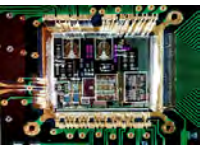
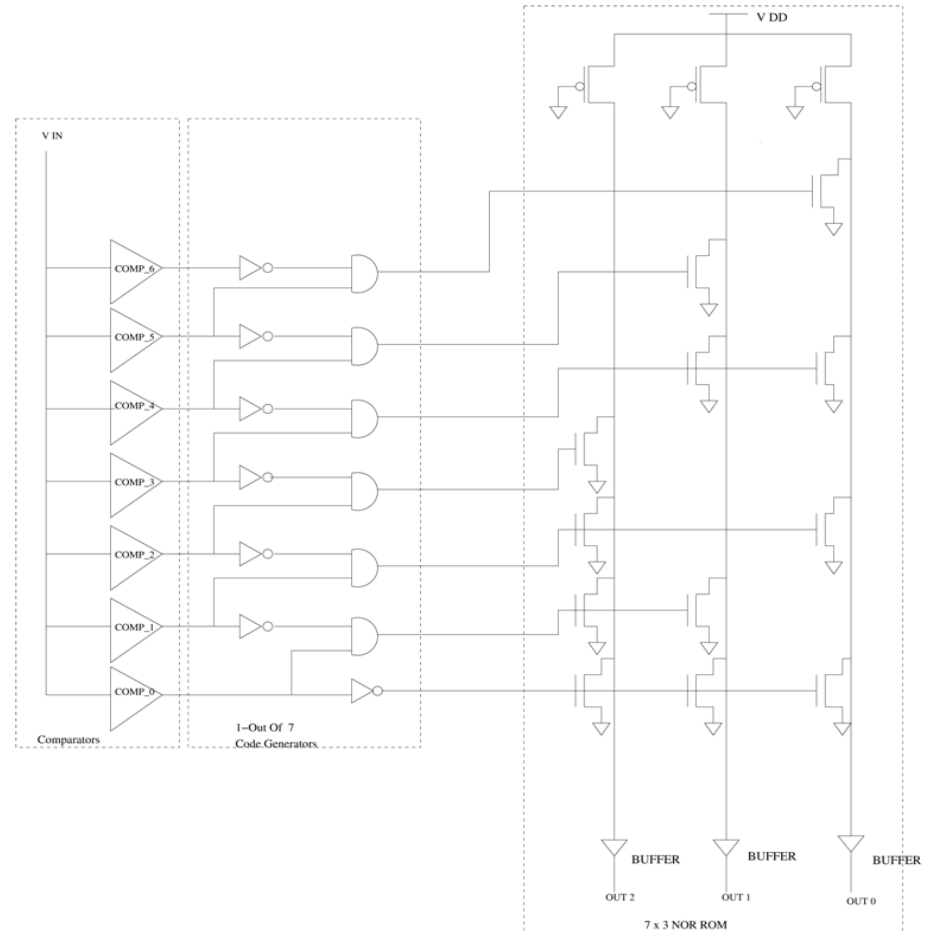
- For an n-bit ADC we need:
 $2^n - 1$ Comparators.
- 1-out of n code generators.
- NOR ROM : $2^n - 1 \times n$.
- For discussion purposes, 3-bit flash ADC is shown. 6-bit ADC has similar structure.



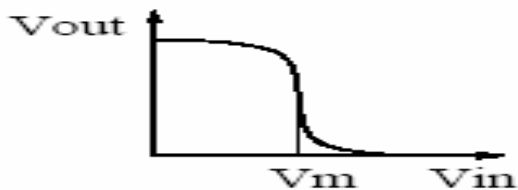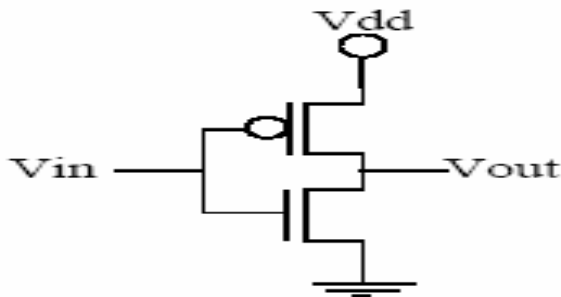
Threshold Inverter Quantization Principle



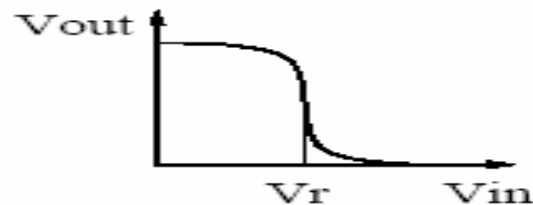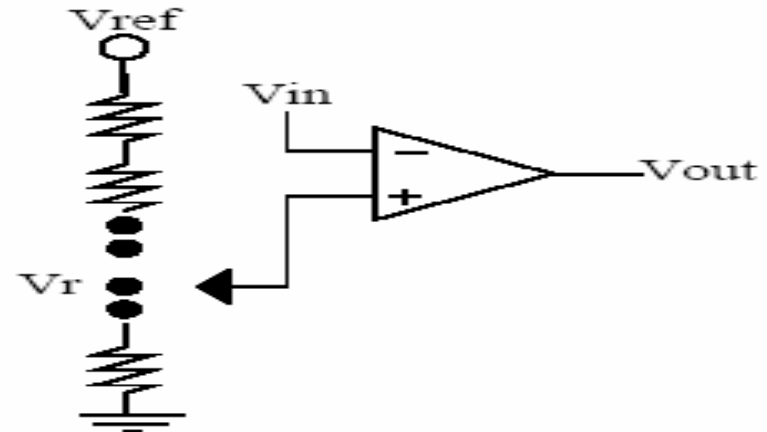
- TIQ comparator.
- Formed by cascading of digital inverters.
- Sizing of transistors determine switching point.



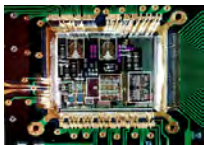
- Differential comparator.
- Require resistive ladder network.
- Area overhead increases.




TIQ Comparator

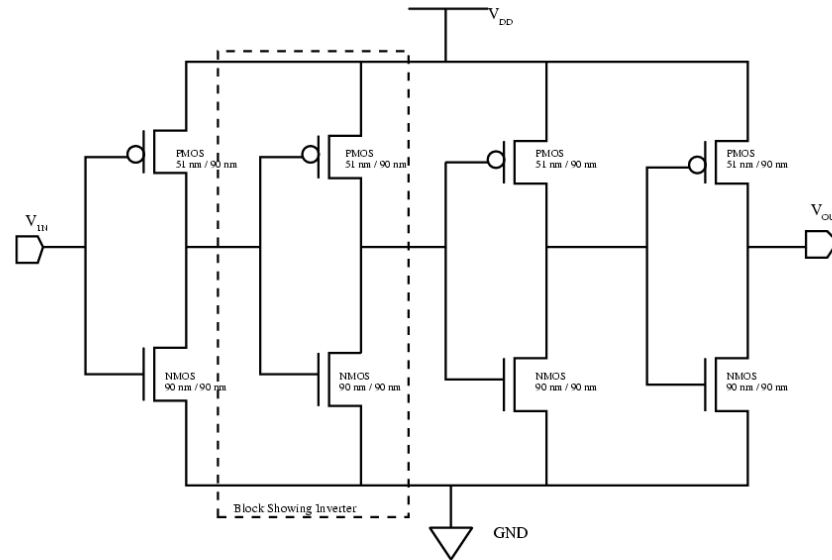

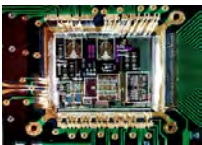- ❑ Formed by four cascaded inverters.
- ❑ Provide a sharper switching for the comparator and full voltage swing.
- ❑ Sizes of PMOS and NMOS in a comparator are same, but different for different comparators.




Transistor sizing

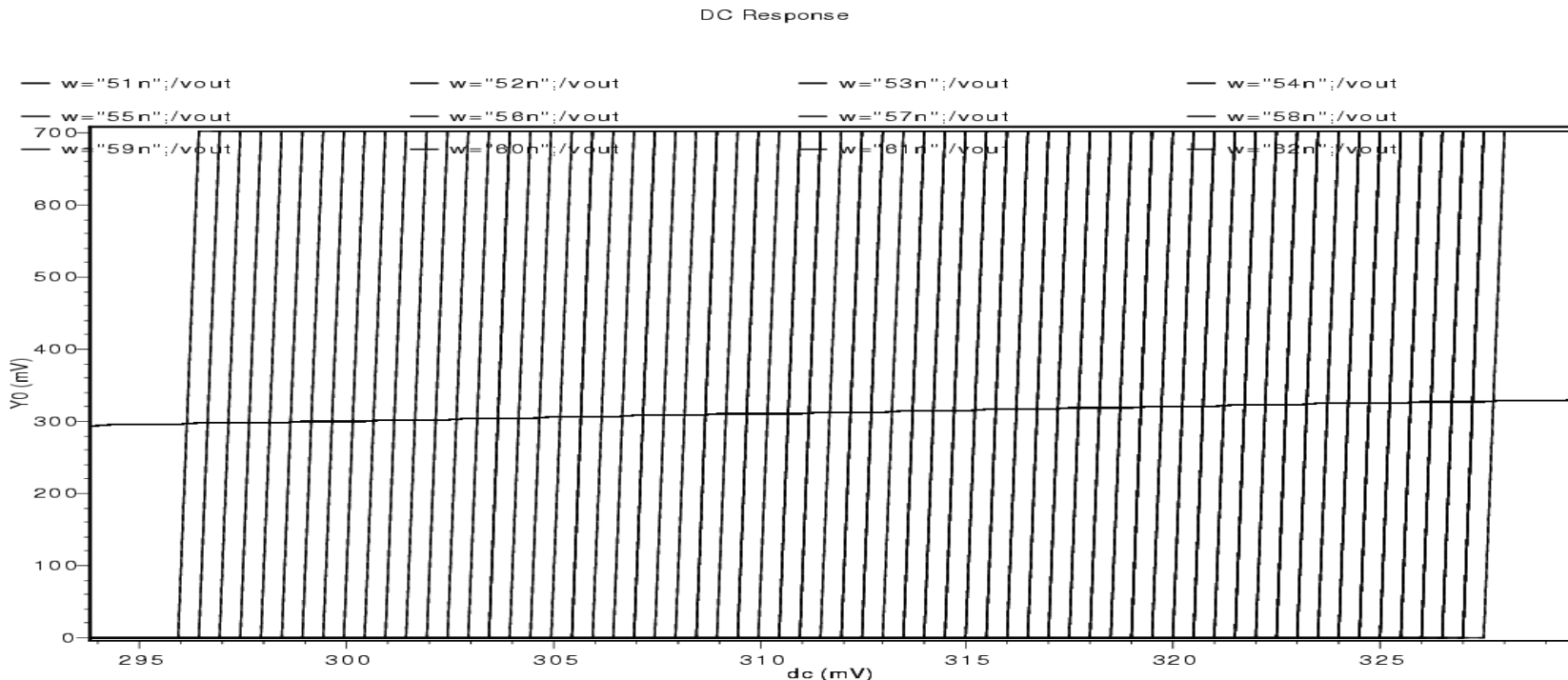

- DC parametric sweep is used to determine the transistor sizes.
- Input voltage varied from 0 to 0.7V in steps of $500\mu V$.
- W/L for NMOS transistors kept as $90nm/90nm$. L for PMOS transistors kept as $90nm$. W for PMOS transistors was given a parametric sweep in steps of $1nm$. Minimum width= $51nm$, maximum width= $163nm$.




Functional Simulation

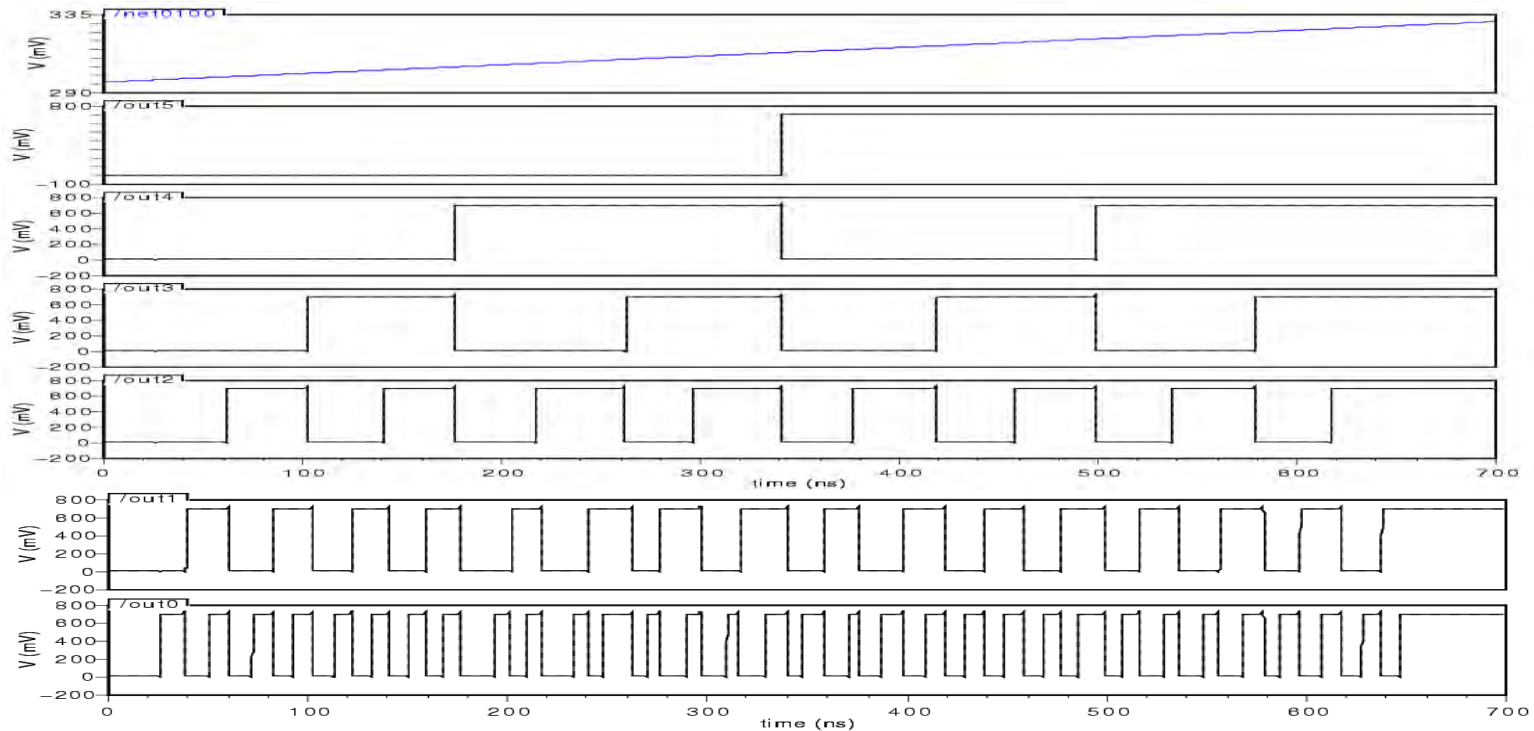


- Transient analysis carried out.
- Ramp generated from $296.3mV$ to $327.8mV$. Digital codes going from 0 to 63 are obtained at the output.




Ideal vs Actual Characteristics

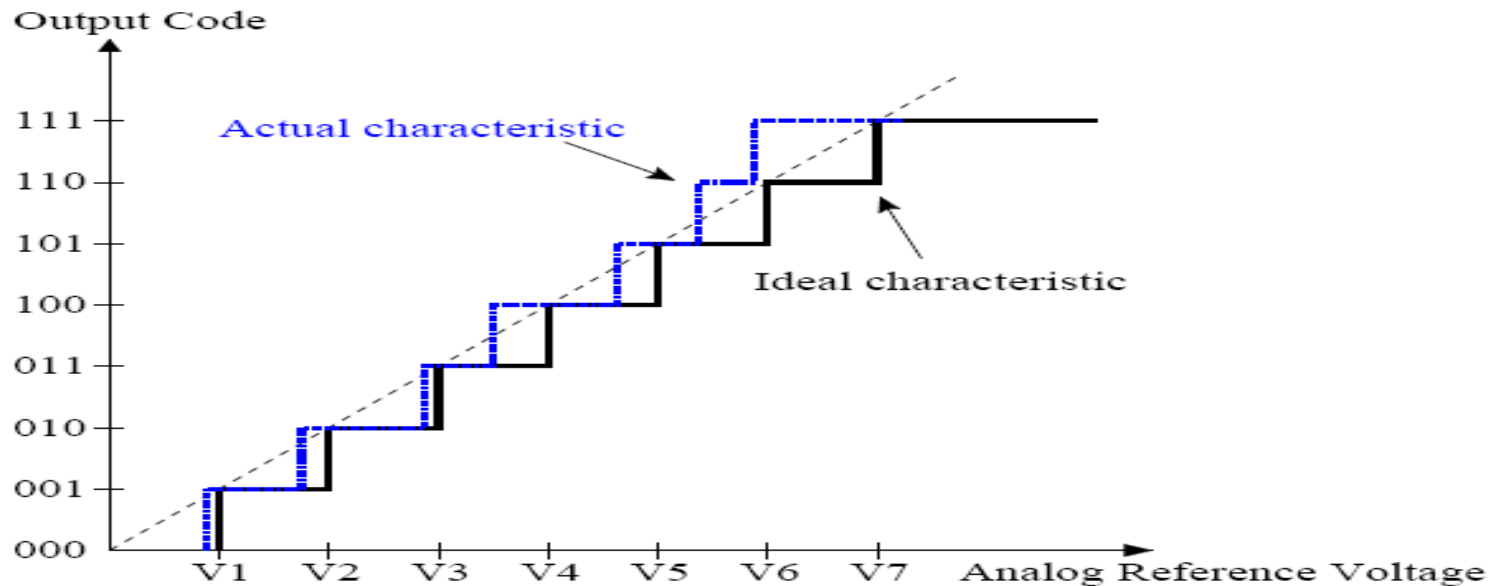

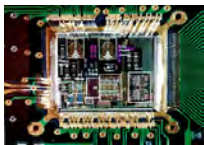- Ideal vs actual transfer function
- Due to transistor implementation, actual transfer function never equal to ideal transfer function.
- Characterized using DNL and INL.




Max DNL of ADC = $0.7LSB$

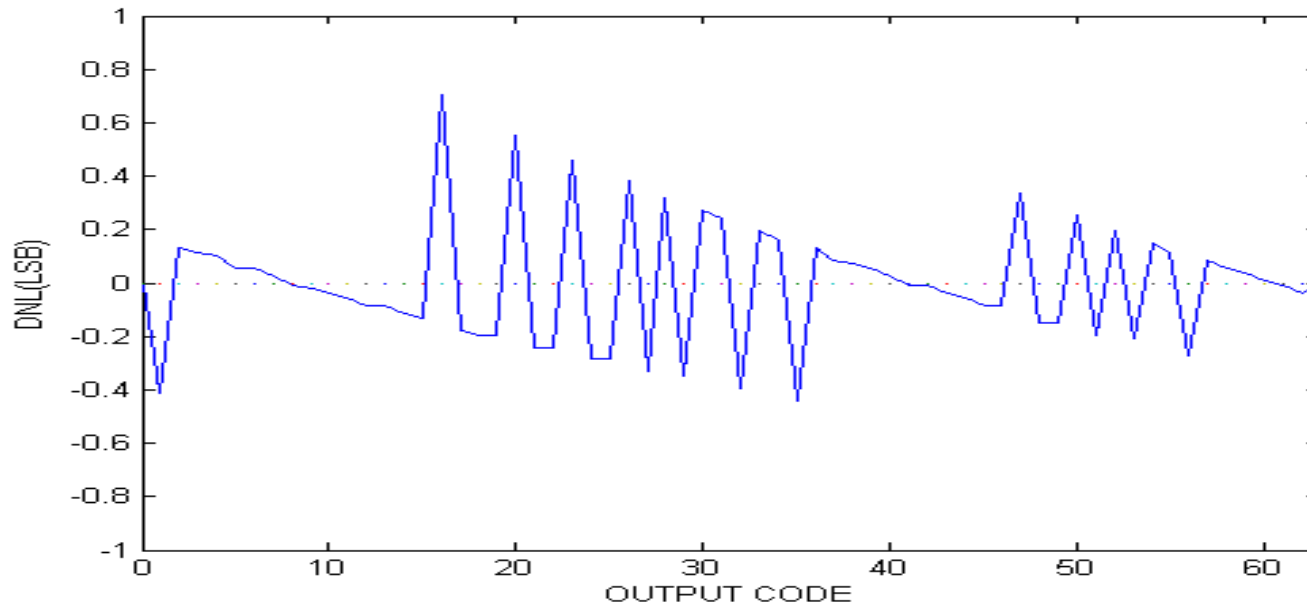


- Differential Non-Linearity. Difference between actual step width and ideal value of 1LSB.
- Modeled as Verilog-A block. Uses histogram method. $DNL < 1LSB$ ensures monotonicity.




Max INL of ADC = $0.46LSB$

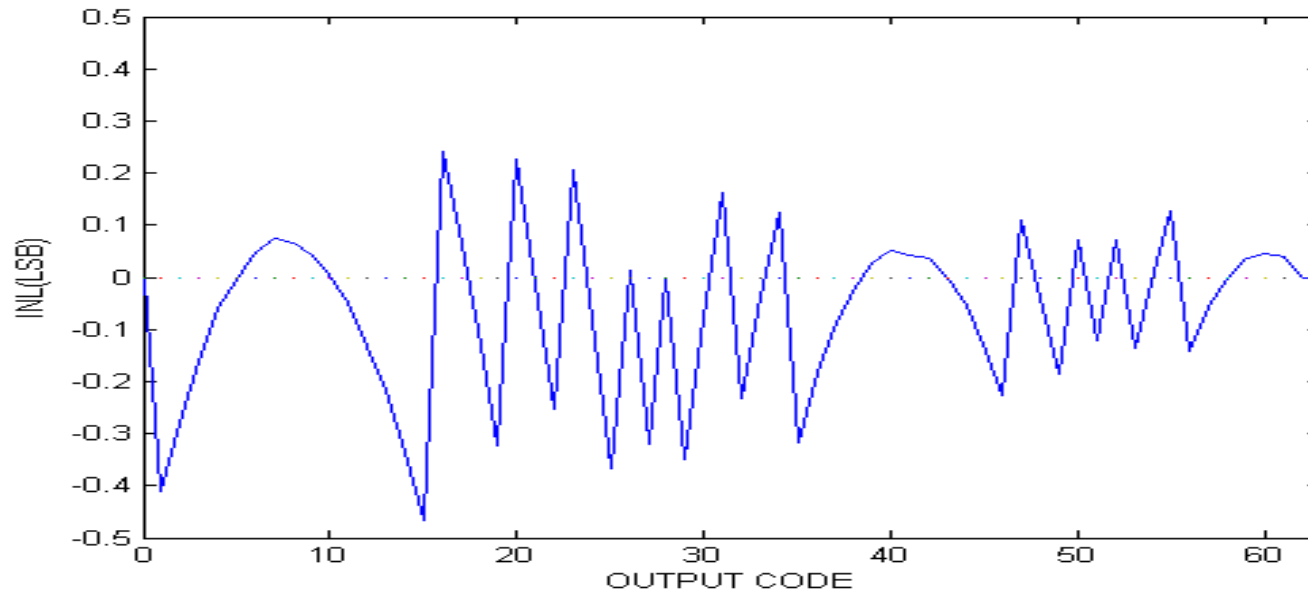

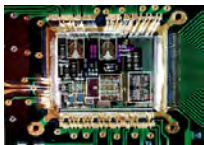- Integral Non-linearity. Deviation of actual transfer function from a straight line. expressed in *LSB*.
- Verilog-A block used. Slowly varying ramp given as input, covering full scale range in 4096 steps.




$$\text{SNDR} = 31.9\text{dB}$$

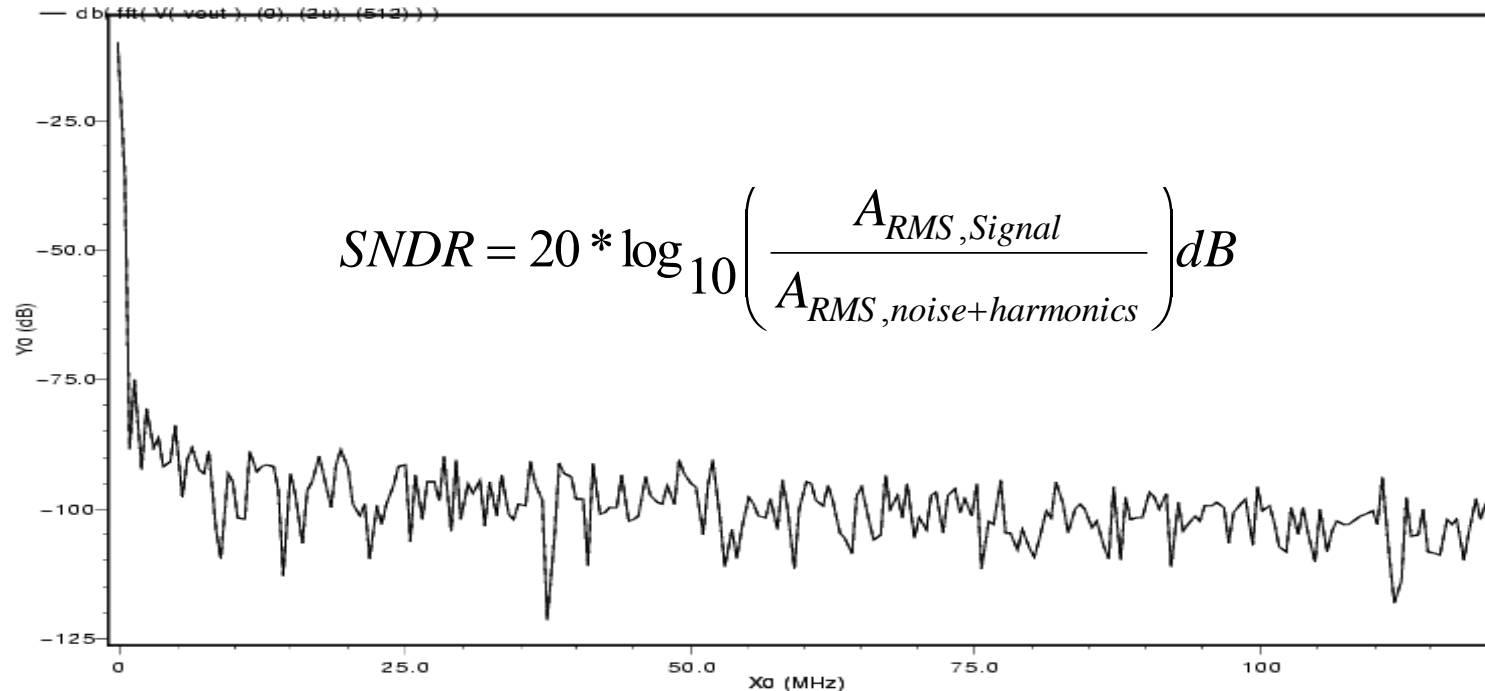


- Signal to noise and distortion ratio.
- ADC output fed to Ideal DAC. FFT of DAC output obtained. SNDR calculated from this.



Instantaneous Power Plot

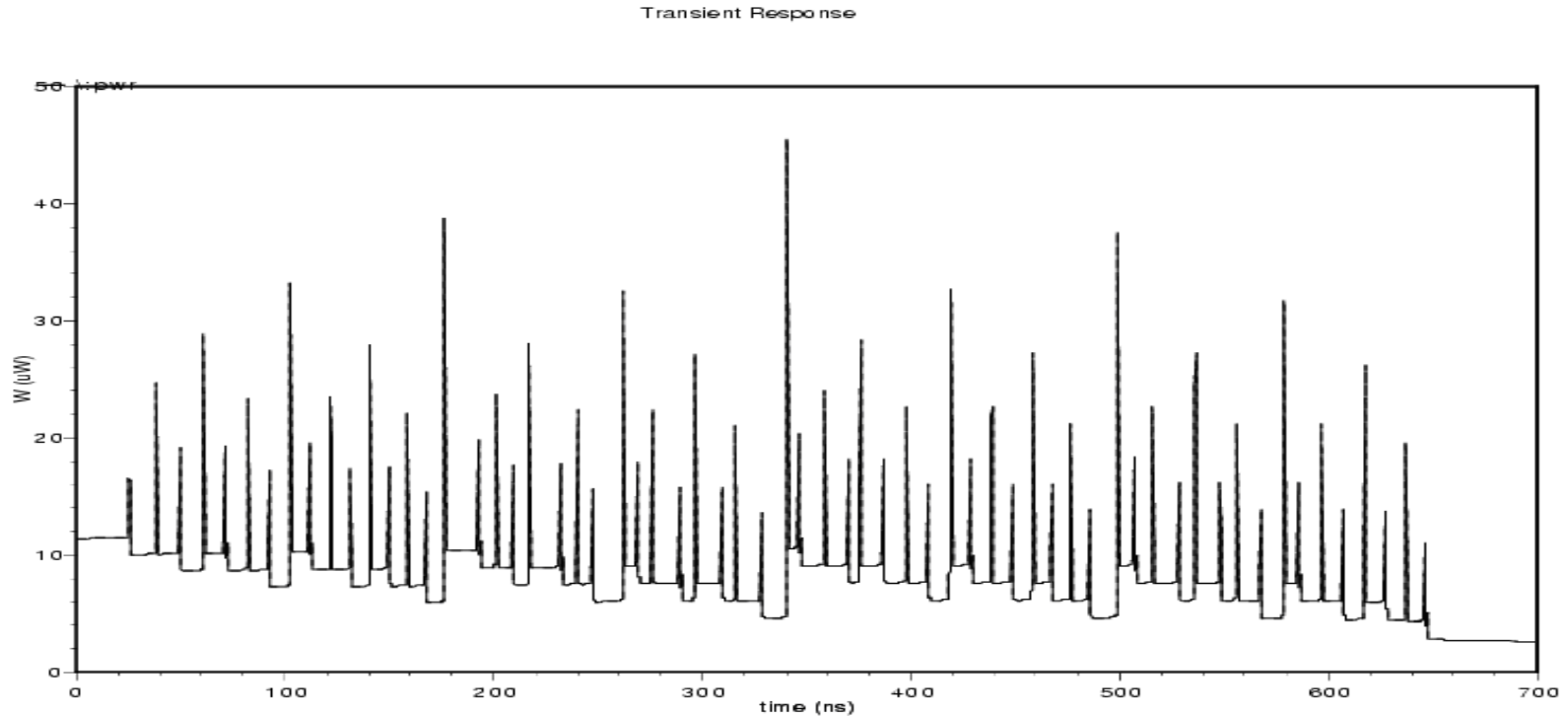

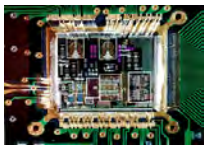- Peak Power= $45.42\mu W$.
- Avg. Power= $8.8\mu W$.
- Low power design.



Conclusions

- Successful ADC design at nano-scale ($45nm$) technology.
- $DNL=0.7LSB, INL=0.46LSB$.
- $SNDR=31.9dB$, Low power design (Avg. Power = $8.8\mu W$).
- Layout using $90nm$ general process design kit.
- Scaling the layout rules to perform layout at $45nm$.



A Process and Supply Variation Tolerant Low Voltage, High Speed ADC




Outline of the Talk

- Introduction and Motivation
- Contributions, Design issues and Solutions
- Related Prior Research Works
- Transistor level design of the proposed ADC
- Physical design and Characterization of ADC
- Process and Supply variation Characterization
- Conclusion and Future Works



Introduction: Why Nano-CMOS ADC

- A large number of SoCs manufactured at the *90nm* process, *65nm*, *45nm* closely following.
- Challenge is to meet performance of analog circuit with that of digital portion.
- Systems that once worked at $3.3/2.5V$ need to work at $1.8V$ without performance degradation.
- New circuit design techniques required to accommodate lower supply voltages.
- Analog/Mixed signal circuits should be designed using standard CMOS digital process.

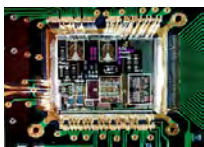


Introduction: Nano-CMOS ADC

- ADC is a true mixed signal circuit used to bridge the gap between analog circuits and digital logic world.
- ADC circuit designs often contain matched transistors. In analog circuits, threshold voltage mismatch needs to be considered.
- For SoC capability, supply voltage variation should also be accounted.
- The demand for emerging application-specific, nanoscale mixed-signal SoCs which need process (threshold voltage mismatch) and power supply voltage variation tolerant ADC interfacing has motivated this research.



Design Issues and Solutions


- Logical and physical design of a **process** and **supply variation tolerant ADC** using **90nm** technology, suitable for SoC integration.
- Post-layout simulation results presented.
- Low supply voltage ($V_{dd} = 1.2V$), low power (Power $\propto V_{dd}^2$). Low V_{dd} puts constraint on the choice of 63 quantization levels (for 6-bit ADC in this paper). $LSB = 1mV$ chosen for this design.
- INL degradation ($INL > 1LSB$) observed in the initial physical design, due to IR drop in the supply lines. $INL = 0.344LSB$, by using large number of contacts and widening the supply lines.
- Power analysis with $100fF$ reveals ADC consumes minimal power.

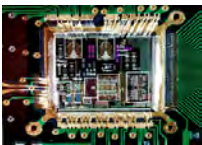


Related Prior Research Works

Works	Tech. (nm)	DNL (LSB)	INL (LSB)	V _{dd} (V)	Power (mW)	Rate (GS/s)
Geelen[9]	350	< 0.7	< 0.7	3.3	300	1.1
Uytttenhove [19]	350	---	---	3.3	---	1
Donovan [6]	250	---	---	2.2	150	0.4
Tseng [8]	250	< 0.1	< 0.4	2.5	35	0.3
Yoo [11]	250	---	---	2.5	66.87	1
Scholtens [16]	180	---	0.42	1.95	328	1.6
Sandner [7]	130	< 0.4	< 0.6	1.5	160	0.6
This Work	90	0.459	0.344	1.2	3.875	1

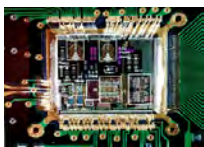
- Low Technology, low voltage, low power, high speed design with satisfactory *DNL*, *INL* performance.



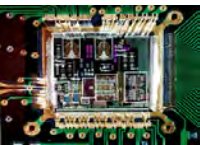
Transistor Level Design of the Proposed ADC




ADC: Block Diagram

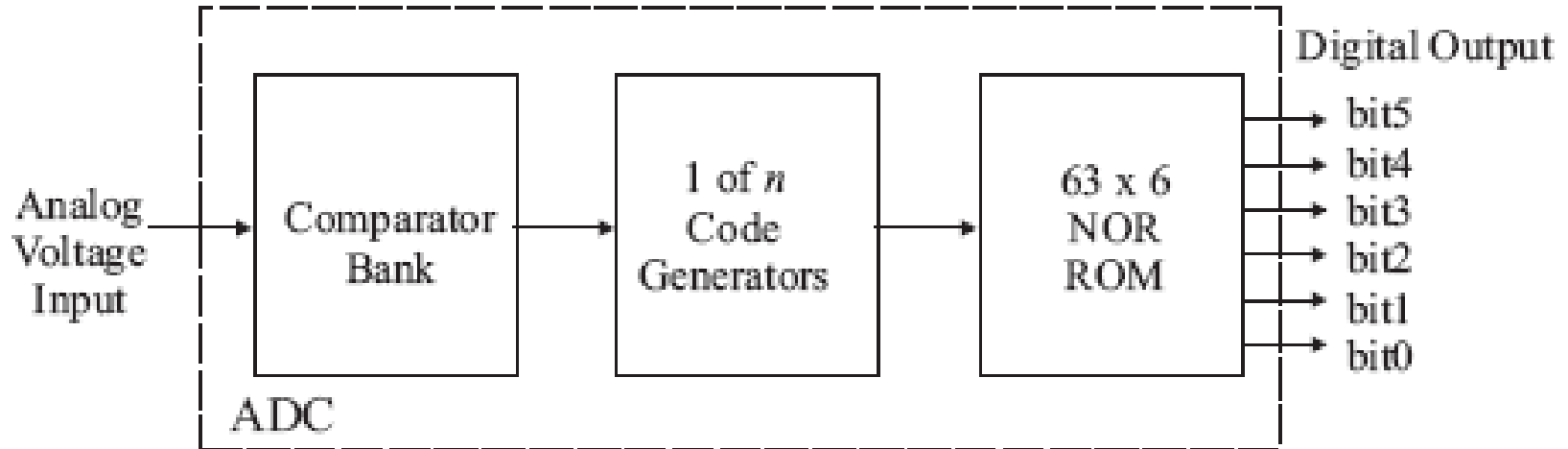

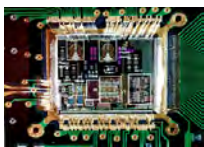- ❑ Output of Comparator Bank is thermometer code.
- ❑ Converted to 1-of n code using 1-of n code generators.
- ❑ NOR ROM converts the 1-of n code to binary code.



ADC : Circuit Diagram

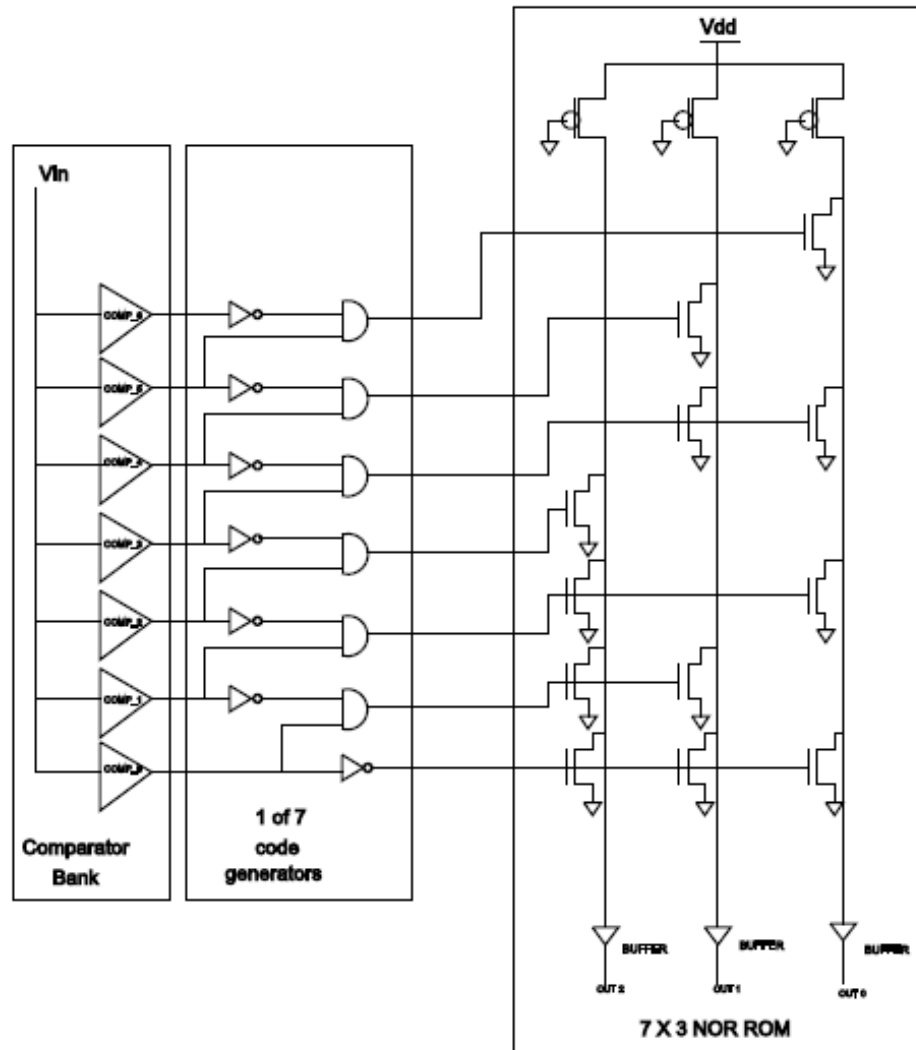


Comparator Design : Technique

- Comparator designed using Threshold Inverting (TI) technique.
- Advantages of TI technique:
 1. High speed.
 2. Simplicity.
 3. Eliminates the need for inherently complex high-gain differential input voltage comparators and additional resistor ladder circuit.



Comparator Design : Circuit

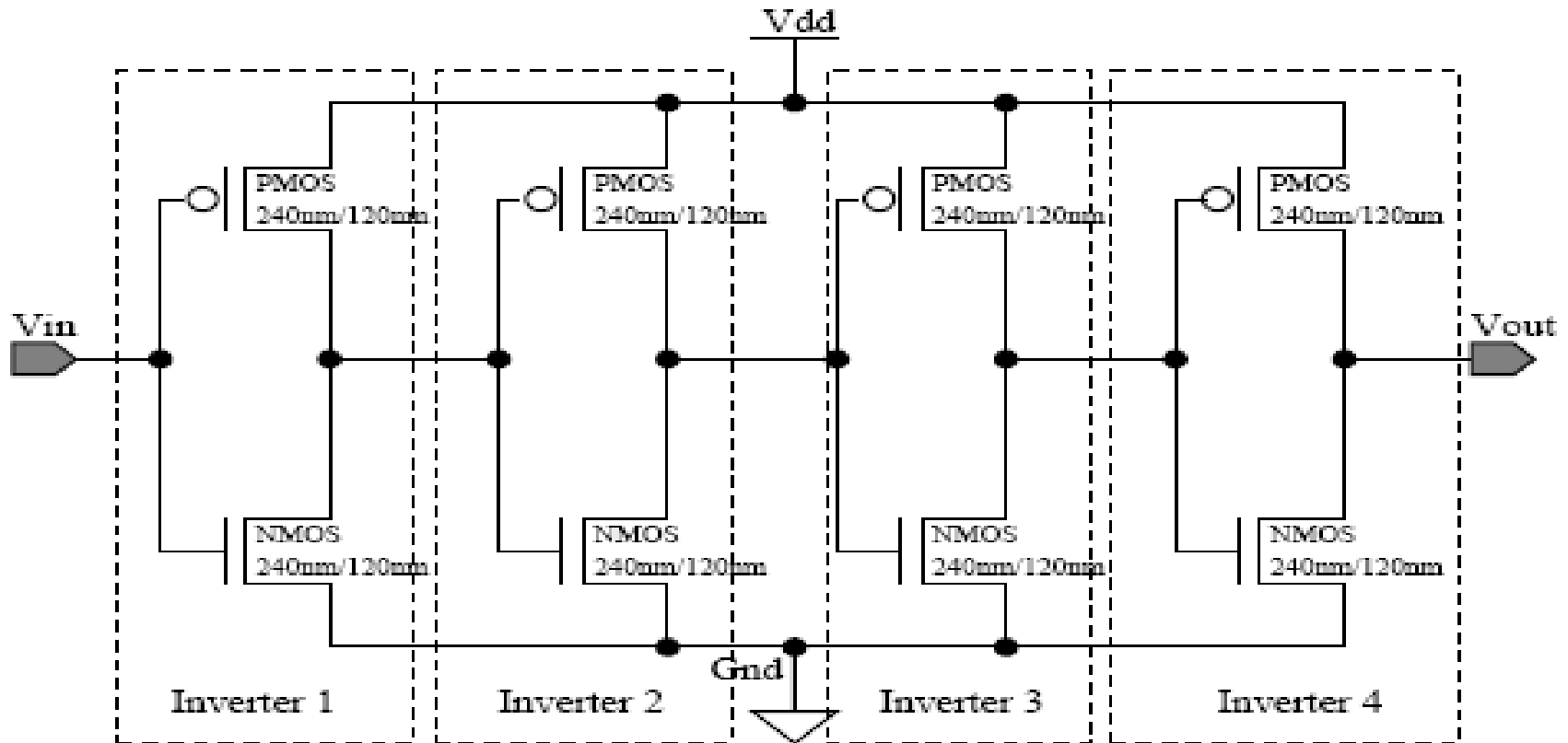

- ❑ $V_{switching}$ set internally based on transistor sizes.
- ❑ Inverter 1 and 2 form the baseline comparator, while Inverter 3 and 4 provide increased gain and sharper switching.



Comparator Design : Equations

For short channel transistors:

$$V_{switching} = V_{dd} \left(\frac{R_n}{R_n + R_p} \right),$$

R_n = NMOS effective switching resistance.
 R_p = PMOS effective switching resistance.

$$InputVoltageRange = V_{dd} - (V_{tn} + |V_{tp}|),$$

V_{dd} = supply voltage.

V_{tn} = NMOS threshold voltage.


V_{tp} = PMOS threshold voltage.

Values chosen $493mV$ to $557mV$.

$$V_{LSB} = \left(\frac{InputVoltageRange}{2^n} \right),$$

For our design,

$$V_{LSB} = 1mV.$$

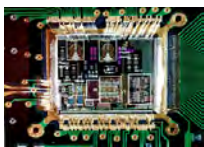

1 of n code generator Design

- Converts thermometer code into 1 of n code.
- Consists of AND gates as combination of an inverter followed by a NAND gate.
- Output from each of the AND gates is fed to the input of the NOR ROM.
- One of the two inputs to the AND gate is fed from the TI comparator output.
- The other input to the AND gate is the inverted output from the next level comparator.




NOR ROM Design

- Converts 1-of-n code to binary code.
- Consists of PMOS (*135nm/180nm*) pull-up and NMOS (*180nm/180nm*) pull-down devices.
- 63 word lines , 6 bit lines, 63 x 6 NOR ROM designed.
- $W_p < W_n$, to ensure PMOS is narrow enough for NMOS to pull down output safely.
- Buffers, consisting of two cascaded inverters (PMOS: *480nm/120nm*, NMOS: *240nm/120nm*) are applied at the outputs to obtain symmetrical waveforms, with equalized rise and fall times.





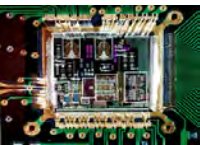Physical Design and Characterization of ADC



ADC: Physical Design

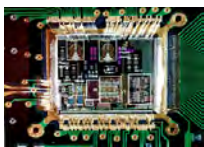
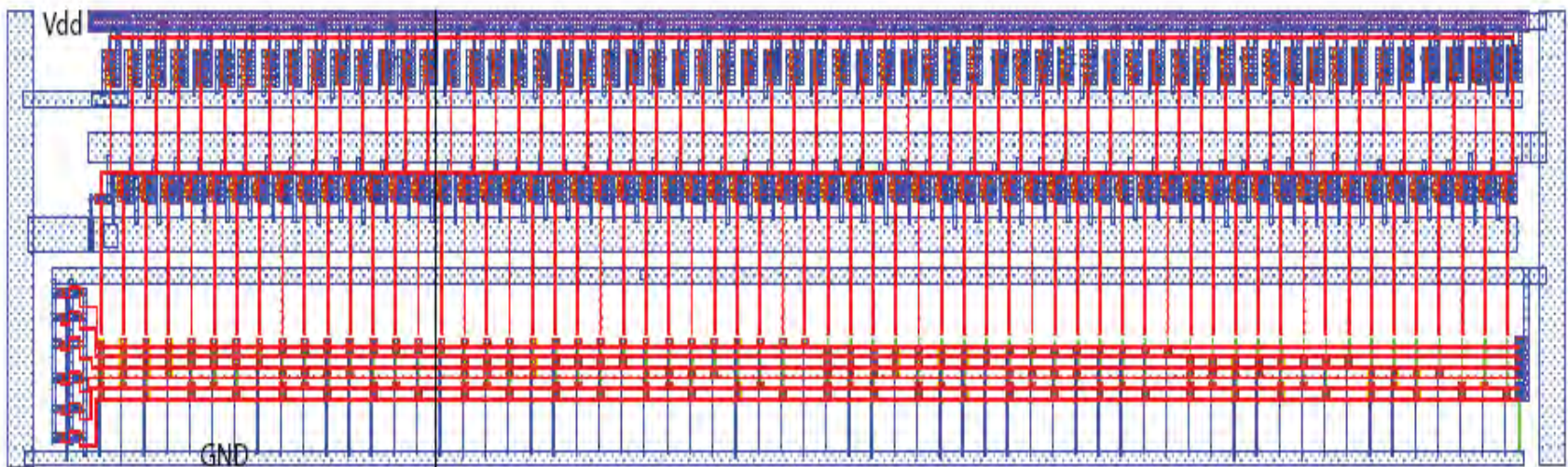
- Physical design of the ADC carried out using 90nm Salicide “1.2V/2.5V 1 Poly 9 Metal” digital CMOS pdk, demonstrating SoC readiness.
- To ensure minimal IR drop, power and ground routing comprises of wide vertical bars and generous use of contacts has been made.



Post Layout Functional Simulation

- Transient analysis is carried out, where a linearly varying ramp covering full scale range of ADC, is given as input.
- Output digital codes from 0 to 63 obtained correctly, with no missing codes. Maximum sampling speed - 1GS/s.

Transient Response

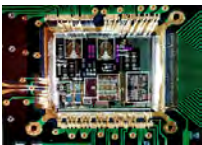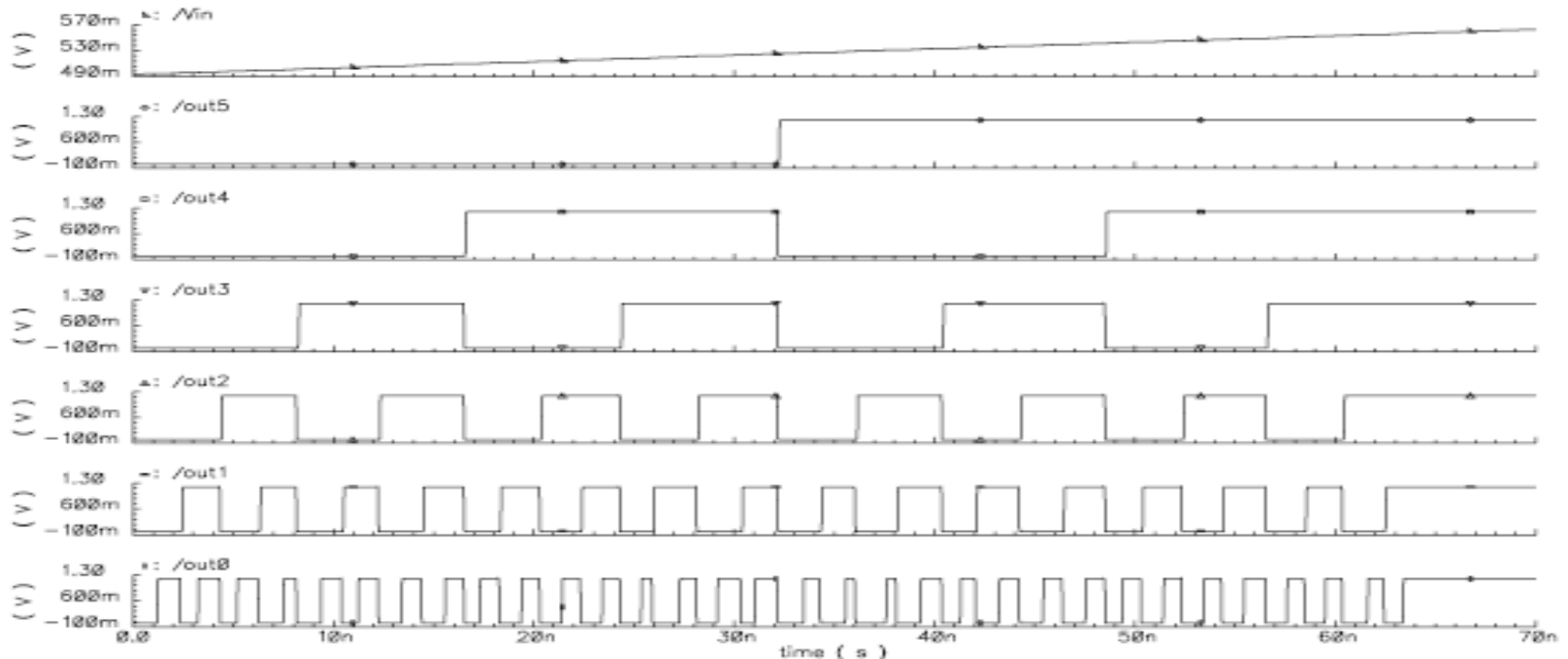

Characterization: Equations


- ADC characterized for static performance.
- Nominal characterization: Histogram test used to determine *INL* (Integral Non-Linearity), *DNL* (Differential Non-Linearity).
- Equations for *INL*, *DNL*:

$$INL[i] = width[i] + INL[i - 1] - 1$$



$$DNL[i] = width[i] - 1$$

$$width[i] = \frac{1 * bucket[i]}{hits * (NUM_{CODES} - 2)}$$

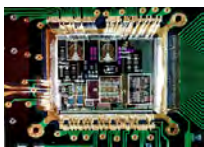- where ***bucket*** holds the number of code hits for each code.
- ***width*** holds the code width calculations.
- Total hits between codes 1 and 62 is denoted as ***hits***.
- ***NUM_{CODES}*** is the number of codes, 64 for a 6-bit ADC.




Characterization: *INL* and *DNL* Plots

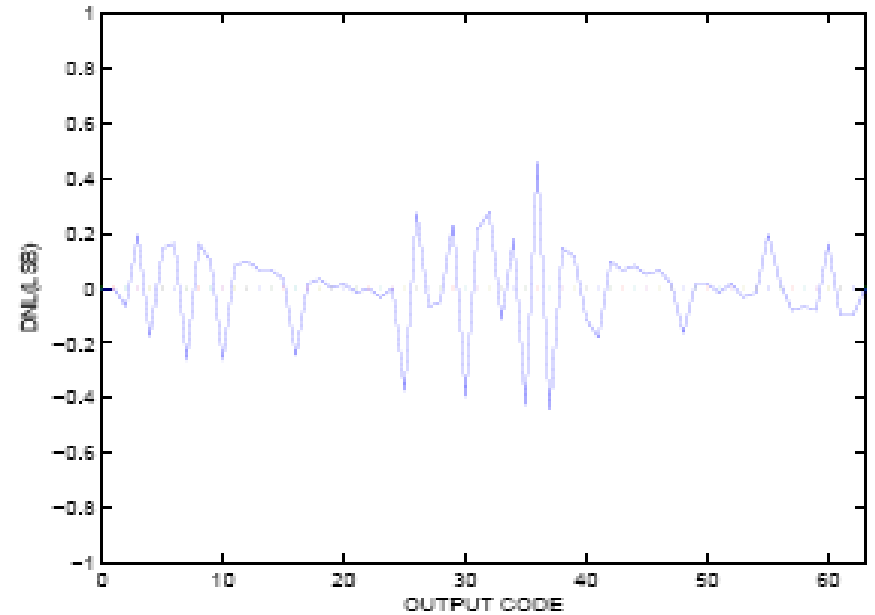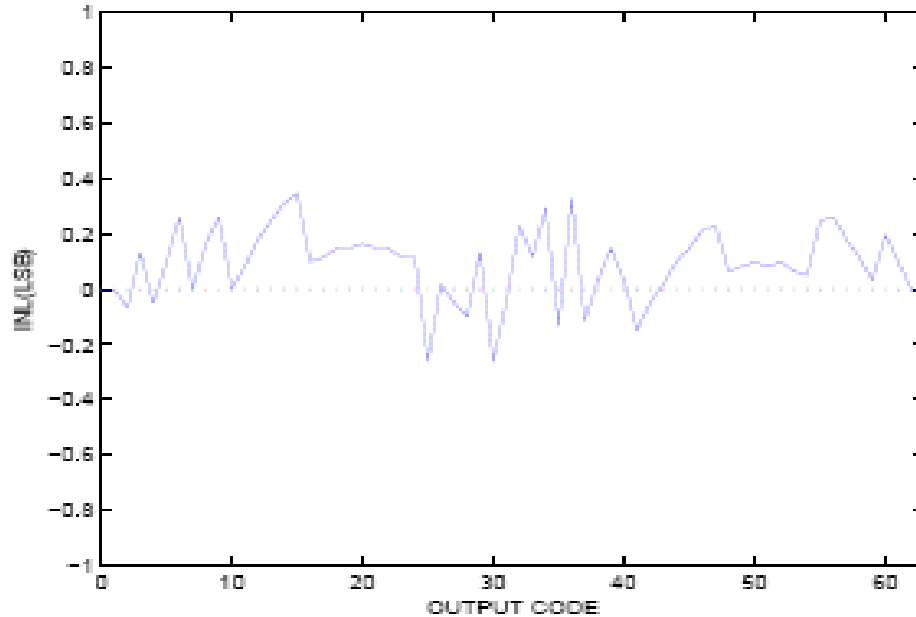

- Maximum $INL=0.344LSB$.
- Maximum $DNL=0.459LSB$.




Power Analysis

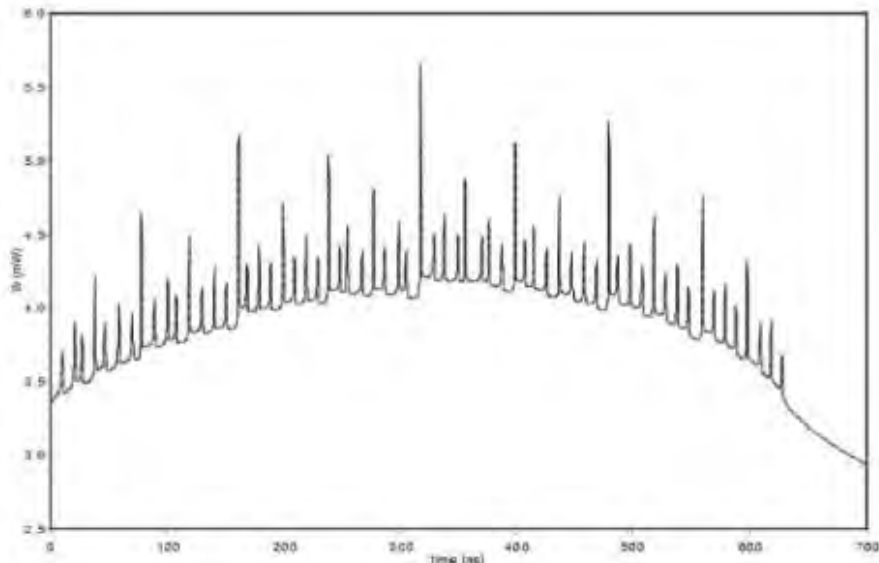

Instantaneous Power Plot.


- Power analysis of the ADC performed with a capacitive load of $100fF$.
- Peak Power = $5.794mW$.
- Average Power = $3.875mW$.

ADC Components	Average Power (mW)
Comparator Bank	3.68125 (95%)
1 of n code Generators	0.03875 (1%)
NOR ROM	0.155 (4%)
Total	3.875

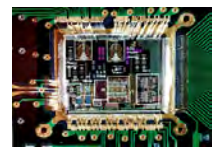

ADC Performance

Parameter	Value
Technology	90nm CMOS 1P 9M
Resolution	6 bit
Supply voltage (V_{dd})	1.2V
Sampling Rate	1GS/s
INL	0.344LSB
DNL	0.459LSB
Peak Power	5.794mW@1.2V
Average Power	3.875mW@1.2V
Input Voltage Range	493mV to 557mV
V_{LSB}	1mV

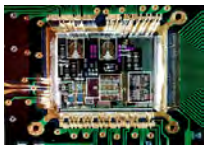

Process and Supply variation Characterization




Process Variation

- Corner-based methodology is used.
- NMOS threshold voltage (V_{tn}) and PMOS threshold voltage (V_{tp}) varied by $\pm 5\%$ from nominal value in the pdk.
- Shift in *INL*, *DNL*, input voltage range recorded.
- *INL* shows maximum variation of 10.5%.
- *DNL* shows maximum variation of 5.7%.




Process Variation: Corner Method

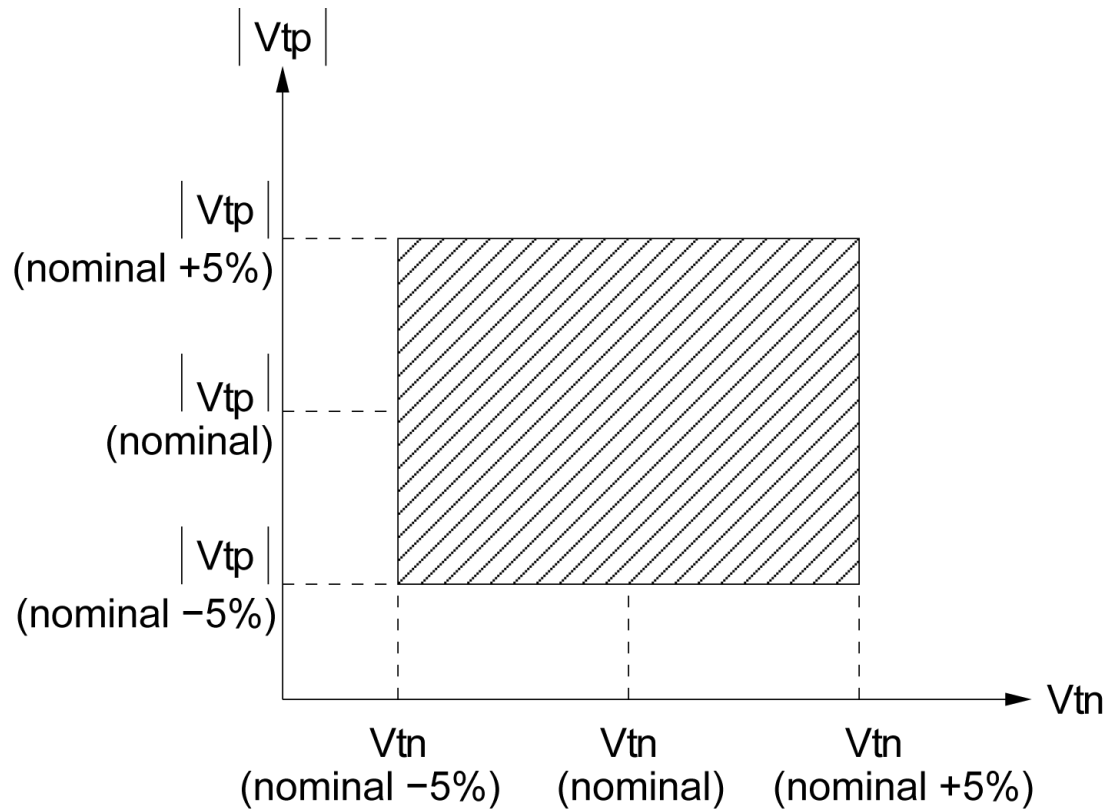

Process Variation: *INL* and *DNL*


<i>V_{tp}</i> , <i>V_{tn}</i>	Input Range (mV)	<i>V_{LSB}</i> (mV)	INL (LSB)	DNL (LSB)
<i>nominal</i>	493-557	1	0.344	0.459
+5%, +5%	495-557	0.96875	0.333	0.46
-5%, -5%	491-556	1.015625	0.345	0.477
-5%, +5%	500-564	1	0.36	0.485
+5%, -5%	501-566	1.015625	0.38	0.479

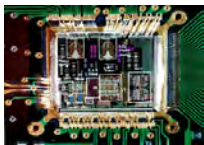

Supply Variation : *INL* and *DNL*

- Nominal supply voltage ($1.2V$) varied by $\pm 10\%$.
- *INL*, *DNL*, and input voltage range values are recorded.
- *INL* shows maximum variation of 4% .
- *DNL* shows maximum variation of 4.8% .

<i>V_{dd}</i> (V)	Input Range (mV)	<i>V_{LSB}</i> (mV)	<i>INL</i> (LSB)	<i>DNL</i> (LSB)
1.08V (-10%)	448-500	0.8125	0.359	0.467
1.2V (nominal)	493-557	1	0.344	0.459
1.32V (+10%)	537-614	1.203	0.339	0.481

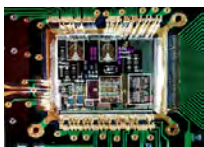

Conclusion and Future Works

- Design of a process and supply variation aware low voltage, high speed flash ADC presented.
- Comparators designed using threshold inverting (TI) technique.
- ADC subjected to $\pm 10\%$ supply variation, $\pm 5\%$ threshold voltage mismatch.
- Nominal $INL=0.344LSB$, maximum variation of 10.5% .
- Nominal $DNL=0.459LSB$, maximum variation of 5.7% .
- It is demonstrated that the design of low voltage, high speed and SoC ready ADCs is possible at $90nm$ technology and below.
- We plan to carry out the complete design cycle for this ADC at $45nm$.
- Alternative encoder architectures will be explored to achieve higher sampling speeds.

