

Combinational Logic Circuits

Instructor: Saraju P Mohanty

(Part 1)

- Binary Logic and Logic Gates (AND, OR, AND)
- Boolean Algebra (Identities, Manipulation, Complement of a Function)
- Standard Forms of Boolean Function (Minterms, Maxterms, SOP, POS)
- Map Specification (Karnaugh Map or K-map)

Digital circuits

- Digital circuits are hardware components manipulating binary information.
- Circuits are implemented using transistors and interconnections in complex semiconductor devices called integrated circuits.
- Each basic circuit is referred to as a logic gate.
- The internal electronics of individual gates are not of our concern, we are only interested in external logic properties.
- Each gate performs specific logic operation and transform input to the output.

Binary Logic


- Binary logic deals with binary variables (that assumes two discrete values) and with the operations applied to these variables.
- Binary variables are designated by alphabets, such as A, B, C, ..., Z.
- The three basic logic operations are AND, OR, and NOT.

| AND | | | OR | | NOT | | |
|-----|---|-----------|----|---|-----------|---|---------------|
| X | Y | Z = X · Y | X | Y | Z = X + Y | X | Z = \bar{X} |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | | |
| 1 | 1 | 1 | 1 | 1 | 1 | | |

Table 2-1 Truth Tables for the Three Basic Logical Operations

Logic Gates

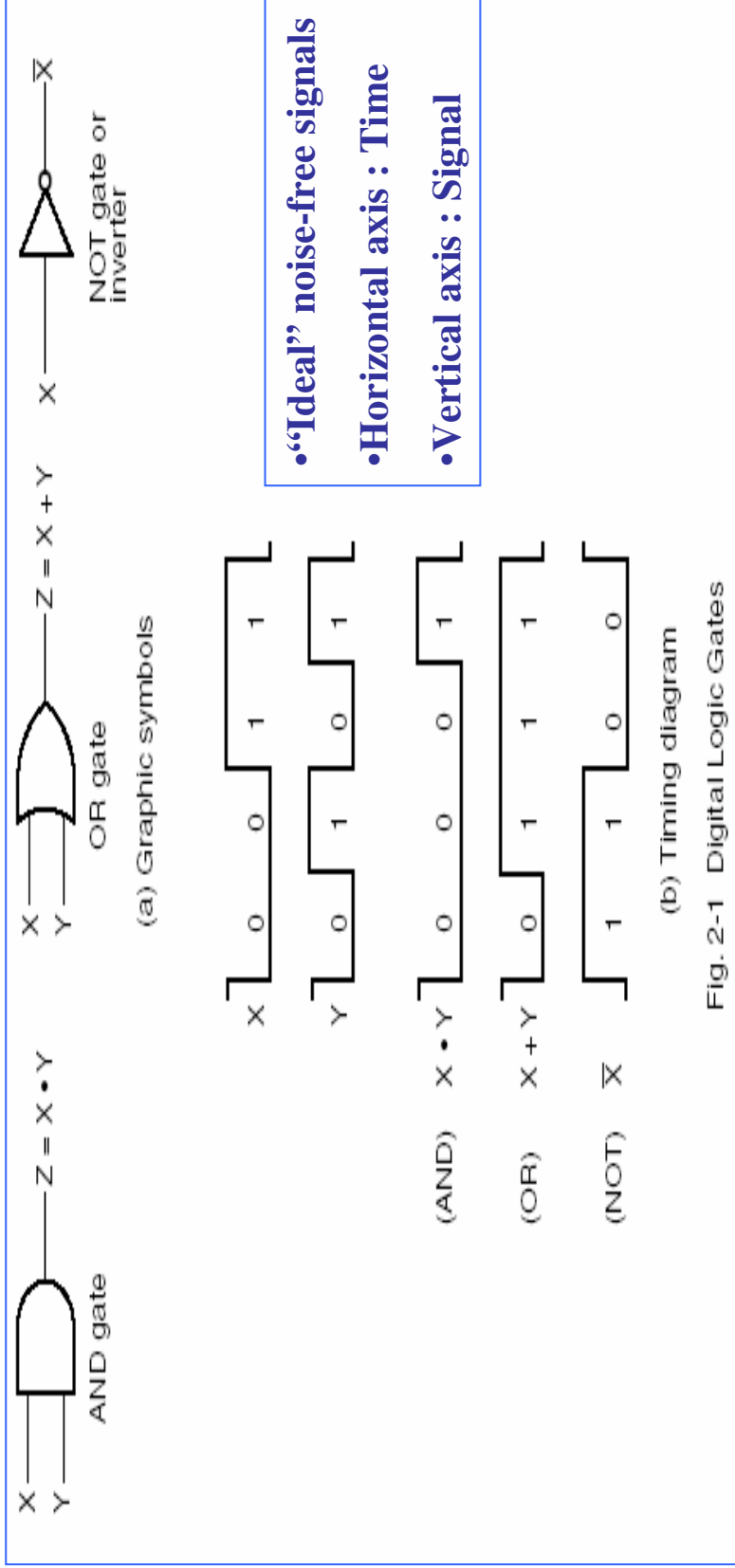- Logic gates are electronic circuits that operate on one or more input signal to produce an output signal.
- Gates can be specified in three different ways: Graphic Symbols, Truth Tables, and Timing Diagrams.



Logic Gates: All basic gates, with NAND and NOR



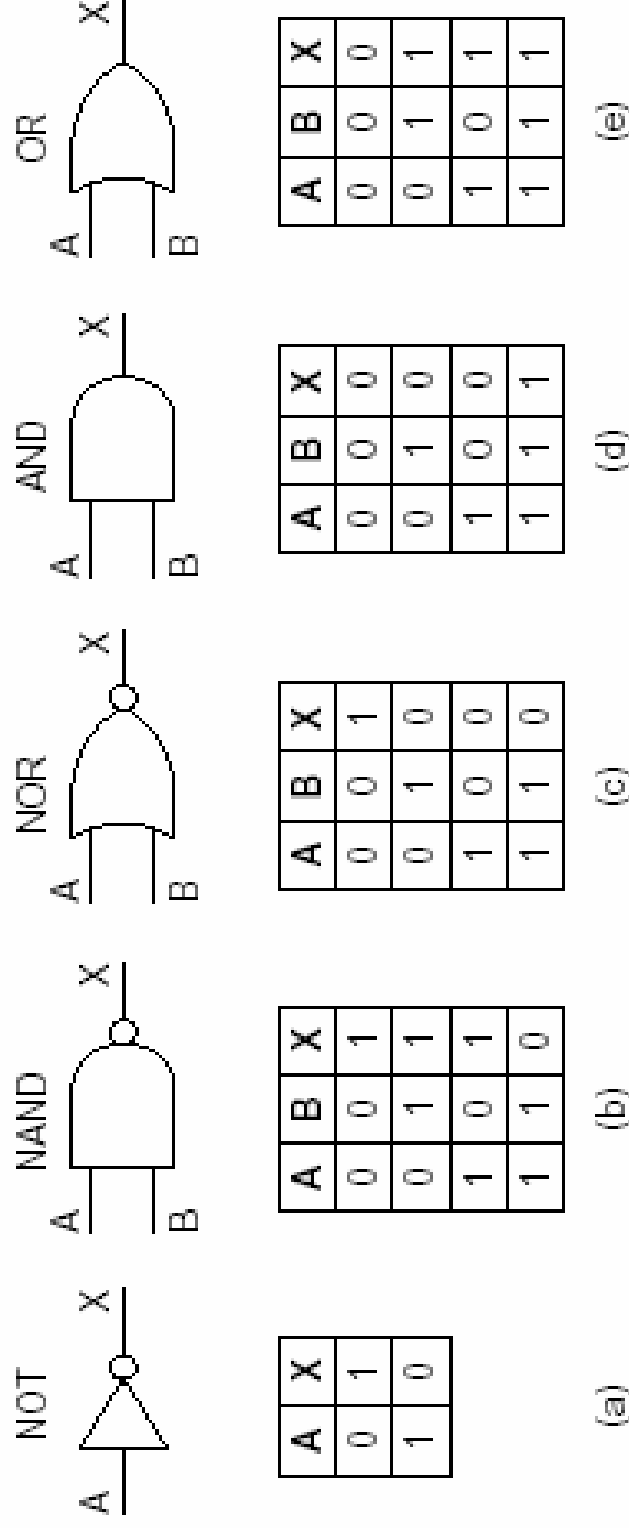


Figure 3-2. The symbols and functional behavior for the five basic gates.

 Logic Gates: Gates with more than two inputs




(a) Three-input AND gate

 

(b) Six-input OR gate

Fig. 2-2 Gates with More than Two Inputs

 

Alternative two input gate design for $F=ABC$

Logic Gates: More on gates...

NOTE: Operationally, **NOR = AND** and **NAND = OR**

 


Figure 3-7. Alternative symbols for some gates: (a) NAND. (b) NOR. (c) AND. (d) OR.

Gates at Transistor Level : BJT


 



Figure 3-1. (a) A transistor inverter. (b) A NAND gate. (c) A NOR gate.

BJT : Bipolar Junction Transistor


Gates at Transistor Level : CMOS FET

 

Inverter

 

NAND

 

NOR

**CMOS FET : Complementary Metal Oxide
Semiconductor Field Effect Transistor**

Boolean Algebra

- To describe the operational properties of digital circuits mathematical notation specifying each gate operation is introduced, which is a class of mathematical system called **Boolean Algebra**.
- For simplicity, the algebra dealing with binary variables and logic properties is Boolean Algebra.
- A **Boolean function** has binary variables, an equal sign and algebraic expression.
- Boolean Function can be represented as a truth table as well.
- For n variable function the number of rows of the truth table will be 2^n .

Boolean Algebra : Boolean Function

- For a given value of binary variables the Boolean function can be equal to either “0” or “1” .
- Example : $F = X + Y'Z$

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Table 2-2 Truth Table for the Function $F = X + \overline{Y}Z$

- The two parts of the algebraic expression, such as “X” and “Y’Z” are called **terms** of the function.

Combinational Logic Circuit ??

- In logic circuits the variables are given as input and the functional value is taken as output.
- The gates are interconnected by wires that carry logic signals.
- Thus, the variables are combined by the logic operations, which gives rise to the name “combinational logic”.
- NOTE: Sequential variables are stored over time and as well as combined.

Boolean Algebra : Some Identities

| Name | AND form | OR form |
|------------------|-------------------------------------|-------------------------------------|
| Identity law | $1A = A$ | $0 + A = A$ |
| Null law | $0A = 0$ | $1 + A = 1$ |
| Idempotent law | $AA = A$ | $A + A = A$ |
| Inverse law | $A\bar{A} = 0$ | $A + \bar{A} = 1$ |
| Commutative law | $AB = BA$ | $A + B = B + A$ |
| Associative law | $(AB)C = A(BC)$ | $(A + B) + C = A + (B + C)$ |
| Distributive law | $A + BC = (A + B)(A + C)$ | $A(B + C) = AB + AC$ |
| Absorption law | $A(A + B) = A$ | $A + AB = A$ |
| De Morgan's law | $\overline{AB} = \bar{A} + \bar{B}$ | $\overline{A + B} = \bar{A}\bar{B}$ |

Some identities of Boolean algebra.

Boolean Algebra : Some Identities

- Nine identities involve single variable.
- Seven identities involve two or more than two variables.
- The duals of an algebraic expression is obtained by interchanging the OR and AND operations, and replacing “1”s by “0”s and “0”s by “1”s.

| | | |
|--|--|--------------|
| 1. $X+0 = X$ | 2. $X \cdot 1 = X$ | |
| 3. $X+1 = 1$ | 4. $X \cdot 0 = 0$ | |
| 5. $X+X = X$ | 6. $X \cdot X = X$ | |
| 7. $X+\bar{X} = 1$ | 8. $X \cdot \bar{X} = 0$ | |
| 9. $\bar{\bar{X}} = X$ | | |
| 10. $X+Y = Y+X$ | 11. $XY = YX$ | Commutative |
| 12. $X+(Y+Z) = (X+Y)+Z$ | 13. $X(YZ) = (XY)Z$ | Associative |
| 14. $X(Y+Z) = XY+XZ$ | 15. $X+YZ = (X+Y)(X+Z)$ | Distributive |
| 16. $\overline{X+Y} = \bar{X} \cdot \bar{Y}$ | 17. $\overline{X \cdot Y} = \bar{X} + \bar{Y}$ | DeMorgan's |

Table 2-3 Basic Identities of Boolean Algebra

Left and right column expressions are duals of each other, for example 10 and 11 are duals each other.

Boolean Algebra : DeMorgan's Theorem

| A) | X | Y | X + Y | $\overline{X+Y}$ | B) | X | Y | \overline{X} | \overline{Y} | $\overline{X} \cdot \overline{Y}$ |
|----|---|---|-------|------------------|----|---|---|----------------|----------------|-----------------------------------|
| | 0 | 0 | 0 | 1 | | 0 | 0 | 1 | 1 | 1 |
| | 0 | 1 | 1 | 0 | | 0 | 1 | 1 | 0 | 0 |
| | 1 | 0 | 1 | 0 | | 1 | 0 | 0 | 1 | 0 |
| | 1 | 1 | 1 | 0 | | 1 | 1 | 0 | 0 | 0 |

Table 2-4 Truth Tables to Verify DeMorgan's Theorem

DeMorgan's Theorem for n variables

- $(X_1 + X_2 + X_3 + \dots + X_n)' = X_1' X_2' \dots X_n'$
- $(X_1 X_2 X_3 \dots X_n)' = X_1' + X_2' + \dots + X_n'$

Boolean Algebra: Algebraic Manipulations

- When Boolean expressions is implemented with logic gates, each term requires a gate, and each variable within the term becomes an input to the gate.
- Example:** Lets consider the implementation of $X + Y'Z$

 


Fig. 2-3 Logic Circuit Diagram for $F = X + \overline{Y}Z$


- Algebraic manipulations are useful for simplifying digital circuits.

Boolean Algebra: Terms and Literals

Literal is a single variable within a term that may or may not be complemented.



3 terms and 8 literals

 

2 terms and 4 literals

Fig. 2-4 Implementation of Boolean Function with Gates

Boolean Algebra: Simplifications

Both (a) and (b) give the same result F:

$$F = X'YZ + X'YZ' + X'Y(Z+Z') + XZ = X'Y + XZ$$

But, (b) needs fewer number of gates, so is area efficient.

 


Fig. 2-4 Implementation of Boolean Function with Gates

Boolean Algebra: Complement of a Function

- Complement of a function is obtained by interchanging “0”s to “1”s and “1”s to “0”s.
- It can be obtained algebraically by applying DeMorgan’s theorem.
- The general DeMorgan’s theorem: Complement of a function can be obtained by interchanging AND and OR operations and complementing each variable and constant.
- Another method of getting complement: Take the dual of the function and complement each literal.

Boolean Algebra: Complementing Example

Find complement of the function, $F = X'YZ' + X'Y'Z$

Method 1: (Using DeMorgan's theorem)

$$\begin{aligned} F' &= (X'YZ' + X'Y'Z)' = (X'YZ')' (X'Y'Z)' \\ &= (X + Y' + Z) (X + Y + Z') \end{aligned}$$

Method 2: (Using Duality)

We have, $F = X'YZ' + X'Y'Z = (X'YZ') + (X'Y'Z)$ (use parentheses to avoid confusion)

Dual of $F = (X' + Y + Z) (X' + Y' + Z)$

Complementing each literal : $(X + Y' + Z) (X + Y + Z') = F'$

Standard Forms of Boolean Functions

- Standard forms help in simplifying the Boolean expressions and frequently results in more desirable logic circuits.
- Standard forms contain **product terms** and **sum terms**.
 - **product terms** (example $X'YZ$)
 - **sum terms** (example $X+Y+Z'$)
- In Boolean algebra, **product** means logical AND operation and **sum** means logical OR operation.
- Two standard forms Standard forms of Boolean functions are:
 - **Sum-of-Products (SOP)**
 - **Product-of-Sums (POS)**
- Product terms are called **minterms** and sum terms are called **maxterms**.

Standard Forms: Minterms

- A product term in which all the variables appear exactly once, either complemented or uncomplemented is called a minterm.
- **Property:** It represents exactly one combination of the binary variables in a truth table. It has the value 1 for that combination and 0 for all others.
- For n variables there are 2^n distinct minterms.
- **Example:** Given two variables X, Y , the four minterms are $X'Y'$, $X'Y$, XY' and XY .
- The symbol for a minterm is m_j , where j denotes the decimal equivalent for which the minterm has the value of 1.

Standard Forms: Minterms (for 3 variables)

| X | Y | Z | Product Term | Symbol | m ₀ | m ₁ | m ₂ | m ₃ | m ₄ | m ₅ | m ₆ | m ₇ |
|---|---|---|-------------------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | $\bar{X}\bar{Y}\bar{Z}$ | m ₀ | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | $\bar{X}\bar{Y}Z$ | m ₁ | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | $\bar{X}Y\bar{Z}$ | m ₂ | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | $\bar{X}YZ$ | m ₃ | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | $X\bar{Y}\bar{Z}$ | m ₄ | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | $X\bar{Y}Z$ | m ₅ | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | $XY\bar{Z}$ | m ₆ | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | XYZ | m ₇ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

Table 2-6 Minterms for Three Variables

The binary numbers from 000 to 111 are listed under variables. For each binary combination there is a related minterm. Each term is the product of exactly 3 literals. A literal is a complemented variable if the corresponding bit of the related binary combination is 0 and it is uncomplemented variable if it is 1. The table is shown above can be extended for any n variables.

Standard Forms: Maxterms

- A **sum** term that contains all the variables in complemented or uncomplemented form is called a **maxterm**.
- For n variables there are 2^n distinct maxterms.
- Each maxterm is the logical sum of the variables, with each variable being complemented if the corresponding bit of the binary number is 1 and uncomplemented if it is 0.
- The symbol for a maxterm is M_j where j denotes the decimal equivalent of the binary combination for which the maxterm has the value 0.
- **Example:** Given two variables X , Y , the four maxterms are $(X+Y)$, $(X+Y')$, $(X'+Y)$, and $(X'+Y')$.

Standard Forms: Maxterms (for 3 variables)

| X | Y | Z | Sum Term | Symbol | M ₀ | M ₁ | M ₂ | M ₃ | M ₄ | M ₅ | M ₆ | M ₇ |
|---|---|---|--|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | $X+Y+Z$ | M ₀ | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | $X+Y+\overline{Z}$ | M ₁ | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | $X+\overline{Y}+Z$ | M ₂ | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | $X+\overline{Y}+\overline{Z}$ | M ₃ | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | $\overline{X}+Y+Z$ | M ₄ | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | $\overline{X}+Y+\overline{Z}$ | M ₅ | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | $\overline{X}+\overline{Y}+Z$ | M ₆ | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | $\overline{X}+\overline{Y}+\overline{Z}$ | M ₇ | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |

Table 2-7 Maxterms for Three Variables

The binary numbers from 000 to 111 are listed under variables. For each binary combination there is a related maxterm. Each term is the sum of exactly 3 literals. A literal is a complemented variable if the corresponding bit of the related binary combination is 1 and it is uncomplemented variable if it is 0. The table is shown above can be extended for any n variables.

Note: $M_j = m_j'$

Standard Forms: Sum-of-Minterms

A function of three variables.

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

A Boolean function can be expressed algebraically by logically summing all the minterms that produce a “1” in the function. This expression is called a “sum of minterms”. The function shown in the left side, can be expressed as follows.

$$\begin{aligned} F &= m_0 + m_2 + m_5 + m_7 \\ &= \Sigma m(0,2,5,7) \end{aligned}$$

The symbol Σ denotes logical sum (OR).

Standard Forms: Product-of-Maxterms

A function of three variables.

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

A Boolean function can be expressed algebraically by finding logical product of all the maxterms that produce a “0” in the function. This expression is called a “product of maxterms”. The function shown in the left side, can be expressed as follows.

$$\begin{aligned} F &= M_1 \cdot M_3 \cdot M_4 \cdot M_6 \\ &= \Pi M(1,3,4,6) \end{aligned}$$

The symbol Π denotes logical product (AND).

Standard Forms: Sum-of-Products and Product-of-Sums

 


Fig. 2-5 Sum-of-Products Implementation

Sum-of-Products (SOP) is the simplified form of the Sum-of-Minterms. An SOP expression is equal to 1 only if one or more of the product terms in the expression is equal to one.

 


Fig. 2-7 Product-of-Sums Implementation

Product-of-Sums (POS) is the simplified form of Product-of-Maxterms. A POS expression is equal to 0 only if one or more of the sum terms in the expression is equal to zero.

Map Simplification

- We need to express a function in simplified form to reduce the number of gates needed for its implementation, thus reducing the overall area of the chip to be fabricated.
- A function has an unique truth table representation, but it can have various algebraic representations.
- Boolean expressions can be simplified by algebraic manipulations, but this is a complicated procedure.
- The map procedure is much simpler.
- The map is known as **Karnaugh map** or **K-map**.
- The K-map is a diagram made up of squares, with each square representing one minterm (or a maxterm) of the function.

Map Simplification: Two-Variable K-Map

| | |
|---|--|
| <p>There are four minterms for a Boolean function with two variables. Hence, the K-map consists of four squares, one for each minterm.</p> | |
| <div> <div> <div> <div> <div></div> <div>m_0</div> </div> <div> <div>m_1</div> <div></div> </div> </div> <div> <div> <div>m_2</div> <div></div> </div> <div> <div>m_3</div> <div></div> </div> </div> </div> <div>(a)</div> </div> <div> <div> <div> <div> <div></div> <div>$\bar{X}\bar{Y}$</div> </div> <div> <div>$\bar{X}Y$</div> <div></div> </div> </div> <div> <div> <div>$X\bar{Y}$</div> <div></div> </div> <div> <div>XY</div> <div></div> </div> </div> </div> <div>(b)</div> </div> | <div> <div> <div> <div> <div></div> <div>0</div> </div> <div> <div>0</div> <div></div> </div> </div> <div> <div> <div>1</div> <div></div> </div> <div> <div></div> <div>1</div> </div> </div> </div> <div>(a) XY</div> </div> <div> <div> <div> <div> <div></div> <div>0</div> </div> <div> <div>0</div> <div></div> </div> </div> <div> <div> <div>1</div> <div></div> </div> <div> <div></div> <div>1</div> </div> </div> </div> <div>(b) $X + Y$</div> </div> |
| <p>Fig. 2-8 Two-Variable Map</p> | |
| <p>Fig. 2-9 Representation of Functions in the Map</p> | |
| <p>$X+Y$ in (b) obtained after simplification.</p> | |

Map Simplification: Three Variable Map

There are eight minterms for a Boolean function with three variables. Hence, the K-map consists of eight squares, one for each minterm.

| | | |
|-------|-------|-------|
| m_0 | m_1 | m_2 |
| m_4 | m_5 | m_6 |

(a)

| <div><div>YZ</div><div>X</div></div> | | Y | | | |
|--------------------------------------|---|-------------------------|-------------------|-------------|-------------------|
| | | 00 | 01 | 11 | 10 |
| X | 0 | $\bar{X}\bar{Y}\bar{Z}$ | $\bar{X}\bar{Y}Z$ | $\bar{X}YZ$ | $\bar{X}Y\bar{Z}$ |
| | 1 | $X\bar{Y}\bar{Z}$ | $X\bar{Y}Z$ | XYZ | $XY\bar{Z}$ |

(b)

Fig. 2-10 Three-Variable Map

Map Simplification: Three Variable Map

(To Remember)

- More than one squares are combined to obtain products with fewer literals.
- One square represents a minterm of three literals.
- A rectangle of two squares represents a product term of two literals.
- A rectangle/square of four squares represents a product term of one literal.
- A rectangle of eight squares covers the entire map and produces a function that is always 1.

NOTE: Similar rules can be formulated for two/four/n-variable K-map.

Map Simplification: Three Variable Map

Example 1

Example: $F(X, Y, Z) = \sum m(2, 3, 4, 5)$

 


Fig. 2-11 Map for Example 2-3

After simplification we obtain, $F(X, Y, Z) = X\bar{Y} + \bar{X}Y$

Map Simplification: Three Variable Map

Example 2

Example: $F(X, Y, Z) = \Sigma m(0, 2, 4, 6)$


 


Fig. 2-13 Product Terms Using Four Minterms


After simplification we obtain, $F(X, Y, Z) = \bar{X} + \bar{Z}$

Map Simplification: Three Variable Map

Example 3

 
 
$$(a) F_1(X, Y, Z) = \sum m(3, 4, 6, 7) \\ = YZ + XZ$$




$$(b) F_2(X, Y, Z) = \sum m(0, 2, 4, 5, 6) \\ = \bar{Z} + X\bar{Y}$$

Fig. 2-14 Maps for Example 2-4

Map Simplification: Three Variable Map

Example 4

 

| | |
|--|--|
| | |
| $F(X, Y, Z) = X'Z + XZ' + XY'$ $= X'Z + XZ' + Y'Z$ | |
| | |
| $F(X, Y, Z) = Z + X'Y$ | |
| | |

Map Simplification: Four Variable Map

There are sixteen minterms for a Boolean function with four variables; the K-map consists of sixteen squares, one for each minterm.

| | | | |
|----------|----------|----------|----------|
| m_0 | m_1 | m_2 | m_3 |
| m_4 | m_5 | m_6 | m_7 |
| m_{12} | m_{13} | m_{14} | m_{15} |
| m_8 | m_9 | m_{10} | m_{11} |

(a)

| | | | | | |
|------|--|-----|----|----|----|
| YZ | | Y | | | |
| WX | $\begin{matrix} 00 \\ 01 \\ 11 \\ 10 \end{matrix}$ | 00 | 01 | 11 | 10 |
| | | | | | |
| | | | | | |
| | | | | | |

X

Z

(b)

Fig. 2-17 Four-Variable Map

Map Simplification: Four Variable Map

(To Remember)

- More than one squares are combined to obtain products with fewer literals.
- One square represents a minterm of four literals.
- A rectangle of two squares represents a product term of three literals.
- A rectangle/square of four squares represents a product term of two literal.
- A rectangle of eight squares represents a product term of one literals.
- A rectangle of sixteen squares covers the entire map and produces a function that is always 1.

Map Simplification: Four Variable Map

Example 1

 
 


Fig. 2-18 Four-Variable Map: Flat and on a Torus to Show Adjacencies

Map Simplification: Four Variable Map

Example 2

 


Fig. 2-19 Map for Example 2-5: $F = \bar{Y} + \bar{W}\bar{Z} + X\bar{Z}$

Map Simplification: Four Variable Map

Example 3

 


Fig. 2-20 Map for Example 2-6: $F = \overline{B}\overline{D} + \overline{B}\overline{C} + \overline{A}C\overline{D}$

Map Simplification: Four Variable Map

Example 4

 


Fig. 2-21 Prime Implicants for Example 2-7: $\overline{A}D$, $B\overline{D}$, and $\overline{A}B$